



Digital Design

“Sequential Logic”

Dr. Cahit Karakuş, February-2018

Objectives of sequential logic

to discuss the difference between **combinational** and **sequential** logic as well as the difference between **asynchronous** and **synchronous** circuits and to show why the operation of synchronous circuits is more predictable, given propagation delays.

- to explain the operation of the common **latches** and **flip-flops**
 - SR or set–reset latch, which may also be called a SR flip-flop
 - D or data flip-flop
 - T or toggle flip-flop
 - JK flip-flop
- to describe clocking and the differences between **positive edge** and **negative edge** triggering and discuss the type of control inputs — active high and active low; asynchronous, jam or direct.


Sequential Logic

- Has **memory**; the circuit stores the result of the previous set of inputs. The current output depends on inputs **in the past** as well as present inputs.
 - The basic element in sequential logic is the **bistable latch** or **flip-flop**, which acts as a memory element for one bit of data.




The Flip Flop




 


S	R	Q	\bar{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

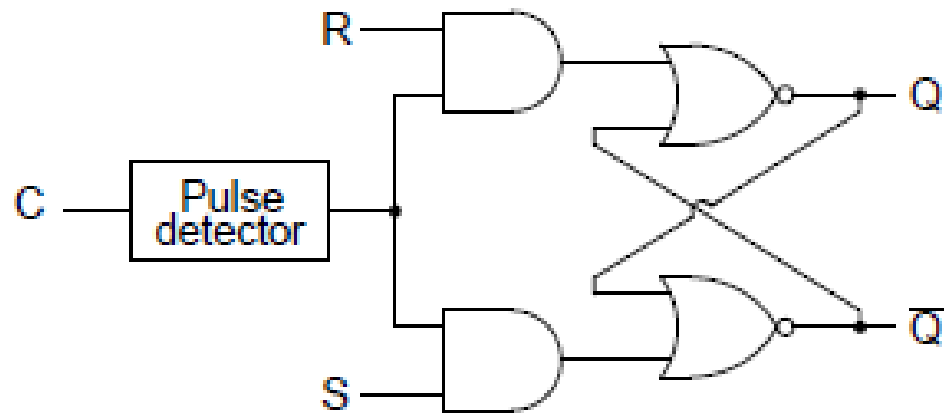

C	S	R	Q	\bar{Q}
\neg	0	0	latch	latch
\neg	0	1	0	1
\neg	1	0	1	0
\neg	1	1	0	0
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch

 


E	D	Q	\bar{Q}
0	0	latch	latch
0	1	latch	latch
1	0	0	1
1	1	1	0

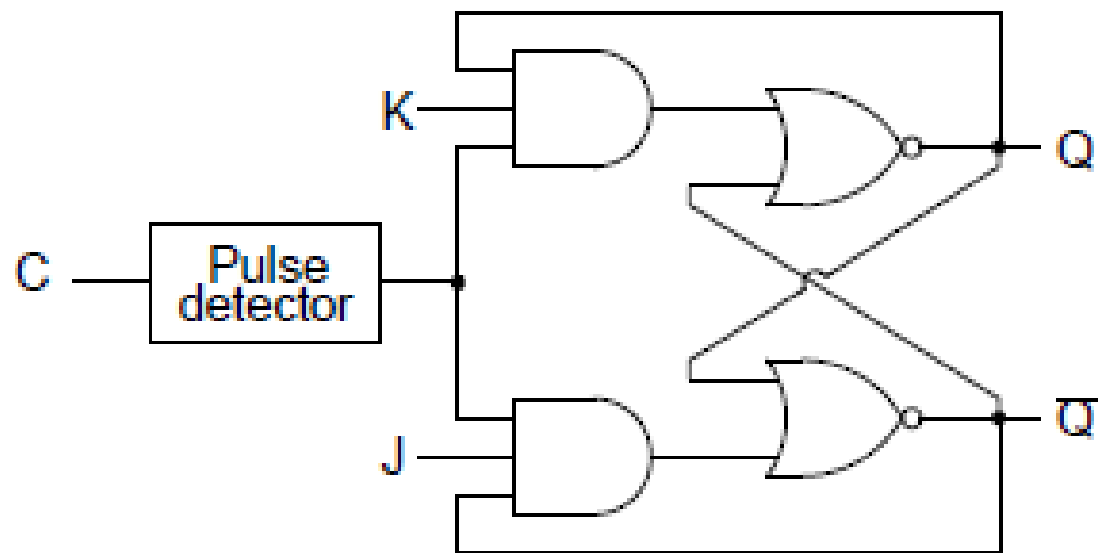

C	J	K	Q	\bar{Q}
┐	0	0	latch	latch
┐	0	1	0	1
┐	1	0	1	0
┐	1	1	toggle	toggle
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch


Flip-flop çeşitleri

 - D flip-flop'u temel alınarak çeşitli flip-floplar tasarlanmıştır.
- **JK flip-flop** (S ve R a benziyor ama JK=11 flip-flop un şimdiki durumunun tümleyenini almak için kullanılır.)




C	J	K	Q_{gelecek}
0	x	x	Değişmez
1	0	0	Değişmez
1	0	1	0 (reset)
1	1	0	1 (set)
1	1	1	$Q'_{\text{şimdiki}}$

 - **T flip-flop** sadece şimdiki durumu tutar veya tümleyenini alır.




C	T	Q_{gelecek}
0	x	Değişmez
1	0	Değişmez
1	1	$Q'_{\text{şimdiki}}$

 
Tüm Flip-Flop(FF)lar için karakteristik tablolar







Q(t)	Q(t+1)	D	İşlem
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

 

Q(t)	Q(t+1)	J	K	İşlem
0	0	0	x	Değişmez/reset
0	1	1	x	Set/tümleyen
1	0	x	1	Reset/tümleyen
1	1	x	0	Değişmez/set

 

Q(t)	Q(t+1)	T	Operation
0	0	0	Değişmez
0	1	1	Tümleyen
1	0	1	Tümleyen
1	1	0	Değişmez

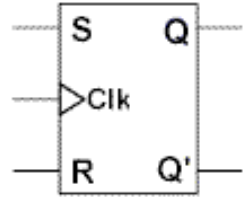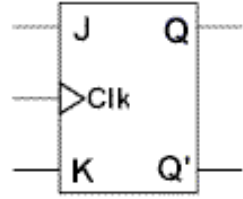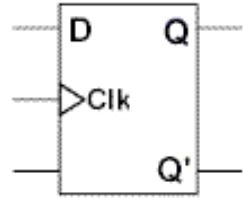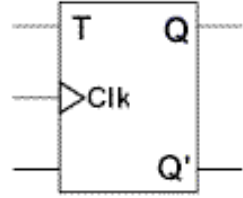FLIP-FLOP NAME	FLIP-FLOP SYMBOL	CHARACTERISTIC EQUATION	EXCITATION TABLE																				
SR		$Q_{(next)} = S + R'Q$ $SR = 0$	<table border="1"> <thead> <tr> <th>Q</th> <th>$Q_{(next)}$</th> <th>S</th> <th>R</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Q	$Q_{(next)}$	S	R	0	0	0	X	0	1	1	0	1	0	0	1	1	1	X	0
Q	$Q_{(next)}$	S	R																				
0	0	0	X																				
0	1	1	0																				
1	0	0	1																				
1	1	X	0																				
JK		$Q_{(next)} = JQ' + K'Q$	<table border="1"> <thead> <tr> <th>Q</th> <th>$Q_{(next)}$</th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> </tr> <tr> <td>1</td> <td>0</td> <td>X</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Q	$Q_{(next)}$	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0
Q	$Q_{(next)}$	J	K																				
0	0	0	X																				
0	1	1	X																				
1	0	X	1																				
1	1	X	0																				
D		$Q_{(next)} = D$	<table border="1"> <thead> <tr> <th>Q</th> <th>$Q_{(next)}$</th> <th>D</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	Q	$Q_{(next)}$	D	0	0	0	0	1	1	1	0	0	1	1	1					
Q	$Q_{(next)}$	D																					
0	0	0																					
0	1	1																					
1	0	0																					
1	1	1																					
T		$Q_{(next)} = TQ' + T'Q$	<table border="1"> <thead> <tr> <th>Q</th> <th>$Q_{(next)}$</th> <th>T</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	Q	$Q_{(next)}$	T	0	0	0	0	1	1	1	0	1	1	1	0					
Q	$Q_{(next)}$	T																					
0	0	0																					
0	1	1																					
1	0	1																					
1	1	0																					


NAME	STATE DIAGRAM
SR	<p>State diagram for SR flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with S, R values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $S, R = 0, 0$ From $Q = 0$ to $Q = 1$: $S, R = 1, 0$ From $Q = 1$ to $Q = 1$: $S, R = 0, 0$ From $Q = 1$ to $Q = 0$: $S, R = 0, 1$
JK	<p>State diagram for JK flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with J, K values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $J, K = 0, 0$ From $Q = 0$ to $Q = 1$: $J, K = 1, 0$ or $1, 1$ From $Q = 1$ to $Q = 1$: $J, K = 0, 0$ From $Q = 1$ to $Q = 0$: $J, K = 0, 1$ or $1, 1$
D	<p>State diagram for D flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with D values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $D = 1$ From $Q = 0$ to $Q = 1$: $D = 1$ From $Q = 1$ to $Q = 1$: $D = 1$ From $Q = 1$ to $Q = 0$: $D = 0$
T	<p>State diagram for T flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with T values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $T = 0$ From $Q = 0$ to $Q = 1$: $T = 1$ From $Q = 1$ to $Q = 1$: $T = 0$ From $Q = 1$ to $Q = 0$: $T = 1$






COUNTERS

Binary count sequence

 - If we examine a four-bit binary count sequence from 0000 to 1111, a definite pattern will be evident in the "oscillations" of the bits between 0 and 1





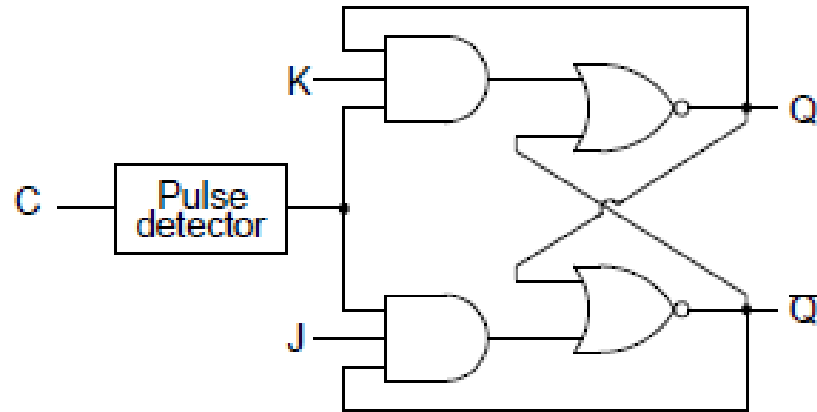 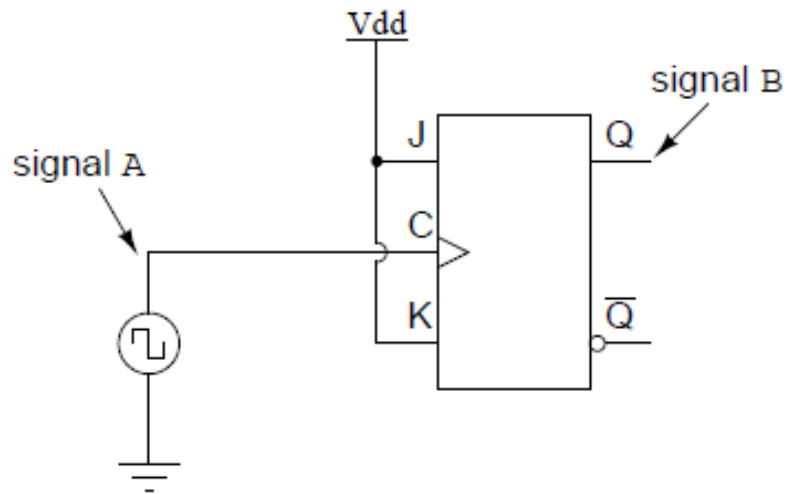0 0 0 0
0 0 0 1
0 0 1 0
0 0 1 1
0 1 0 0
0 1 0 1
0 1 1 0
0 1 1 1
1 0 0 0
1 0 0 1
1 0 1 0
1 0 1 1
1 1 0 0
1 1 0 1
1 1 1 0
1 1 1 1




C	J	K	Q	\bar{Q}
┌	0	0	latch	latch
┌	0	1	0	1
┌	1	0	1	0
┌	1	1	toggle	toggle
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch

A four-bit "up" counter

  

A simultaneous "up" and "down" counter

 

"Up" count sequence


Q_0	0	1	0	1	0	1	0	1	0	1	0	1	0	1		
Q_1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
Q_2	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
Q_3	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

"Down" count sequence

\bar{Q}_0	1	0	1	0	1	0	1	0	1	0	1	0	1	0		
\bar{Q}_1	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0
\bar{Q}_2	1	1	1	1	0	0	0	0	1	1	1	1	0	0	0	0
\bar{Q}_3	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0

Synchronous Counters (continued)

 - Internal details =>
- Internal Logic
 - XOR complements each bit
 - AND chain causes complement of a bit if all bits toward LSB from it equal 1
- Count Enable
 - Forces all outputs of AND chain to 0 to “hold” the state
- Carry Out
 - Added as part of incrementer
 - Connect to Count Enable of additional 4-bit counters to form larger counters




(a) Logic Diagram-Serial Gating



State Table

State Table

- *State table* – a multiple variable table with the following four sections:
 - *Present State* – the values of the state variables for each allowed state.
 - *Input* – the input combinations allowed.
 - *Next-state* – the value of the state at time $(t+1)$ based on the present state and the input.
 - *Output* – the value of the output as a function of the present state and (sometimes) the input.
- From the viewpoint of a truth table:
 - the inputs are Input, Present State
 - and the outputs are Output, Next State

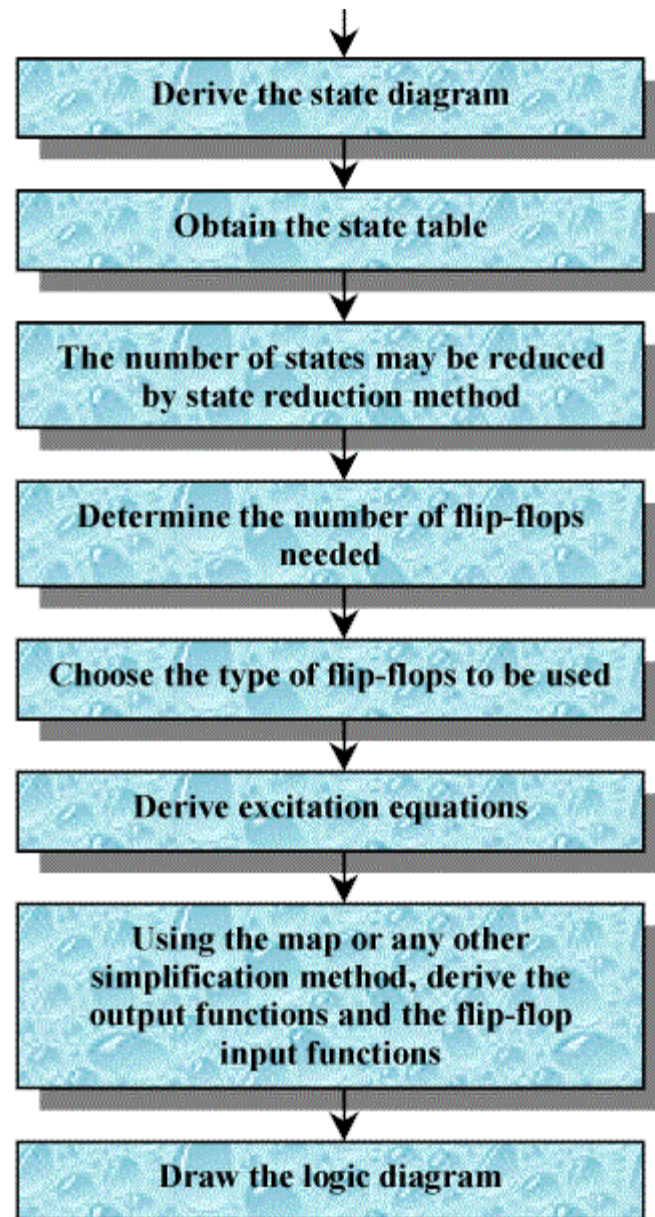

State Table

- The state table can be filled in using the next state and output equations:
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \bar{A}(t)x(t)$;
 - $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Diagrams


- The sequential circuit function can be represented in graphical form as a state diagram with the following components:
 - A circle with the state name in it for each state
 - A directed arc from the Present State to the Next State for each state transition
 - A label on each directed arc with the Input values which causes the state transition, and
 - A label:
 - On each circle with the output value produced, or
 - On each directed arc with the output value produced.





Examples

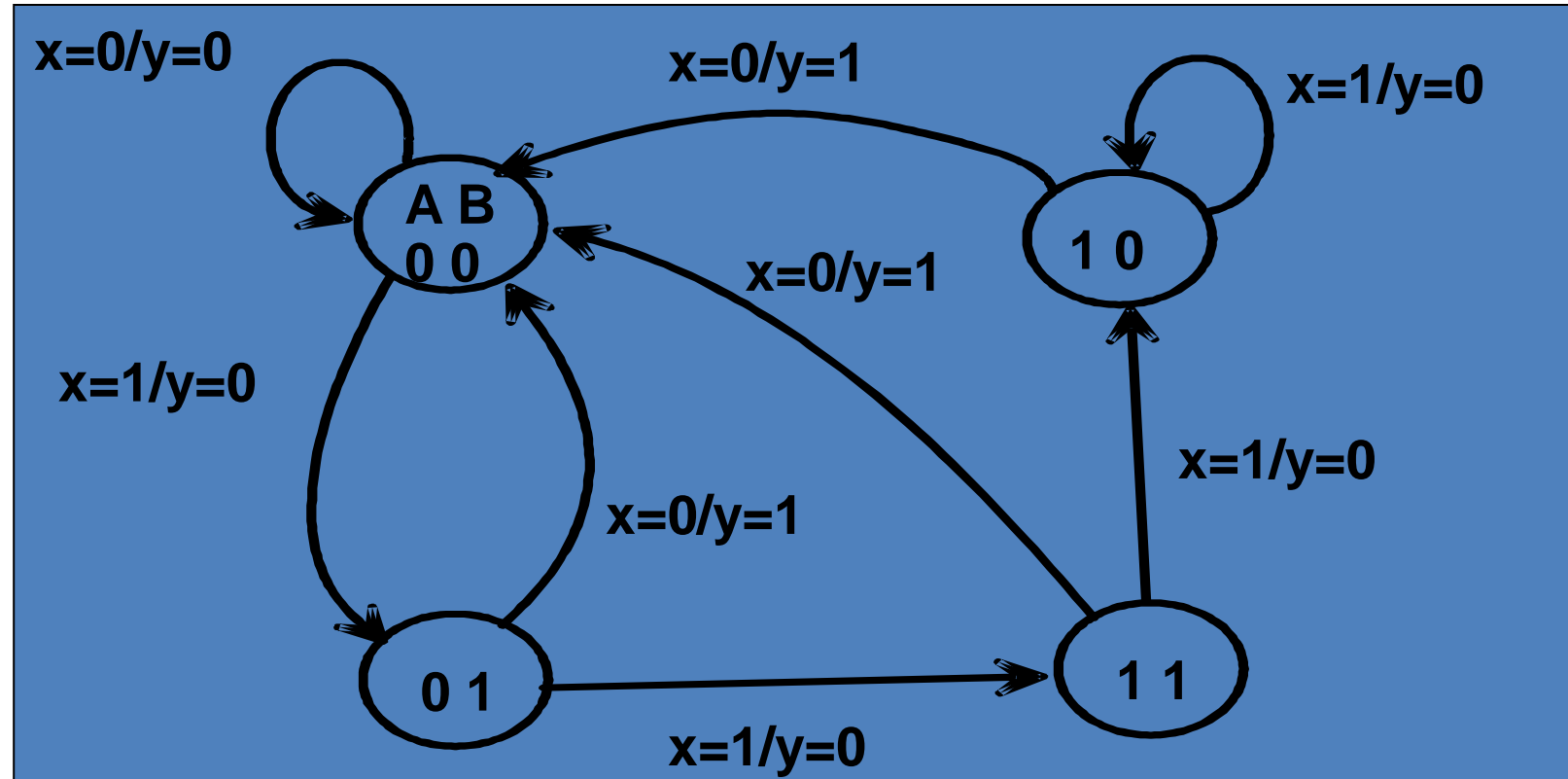Example : State Diagram



- Which type?
- Diagram gets confusing for large circuits
- For small circuits, usually easier to understand than the state table




Registers

 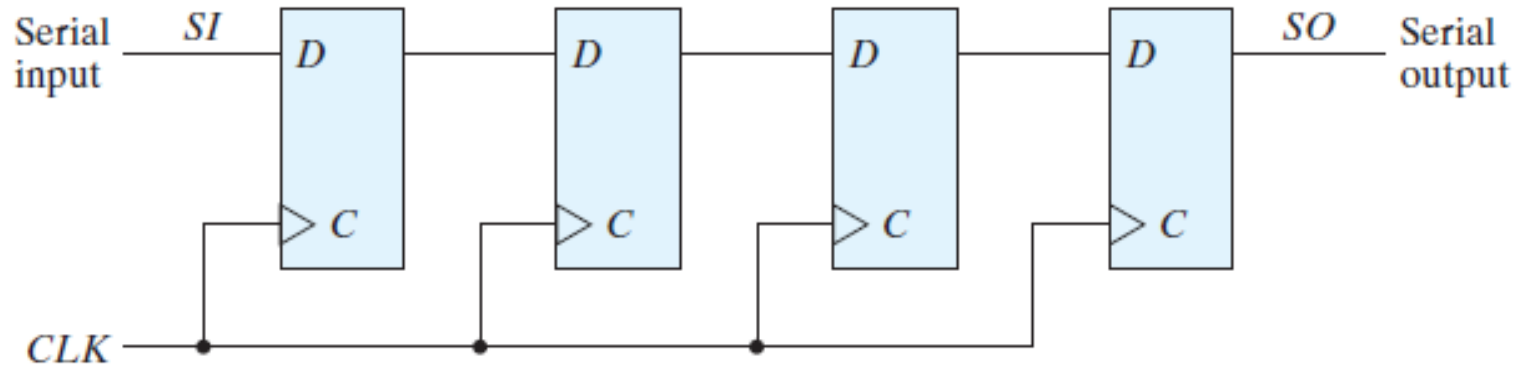

Example: Durum Diyagramı

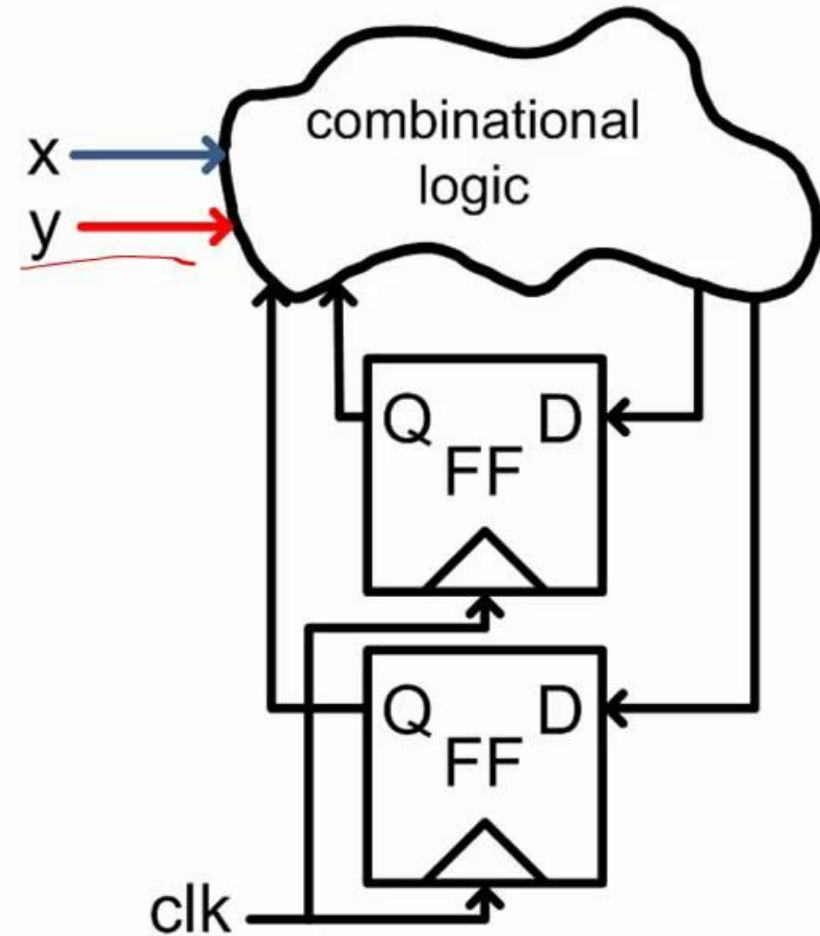 

Example: Sayıcı –JK Flip Flop

 

Tetikleme - Uyarma

Output State Transitions			Flip-flop inputs								
Present State			Next State			J2 K2		J1 K1		J0 K0	
Q2	Q1	Q0	Q2	Q1	Q0						
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

C	J	K	Q	\bar{Q}
┌	0	0	latch	latch
┌	0	1	0	1
┌	1	0	1	0
┌	1	1	toggle	toggle
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch

Q2Q1 \ Q0	0	1
00	0	0
01	0	1
11	X	X
10	X	X

J2 map

Q2Q1 \ Q0	0	1
00	0	1
01	X	X
11	X	X
10	0	1

J1 map

Q2Q1 \ Q0	0	1
00	1	X
01	1	X
11	1	X
10	1	X

J0 map

$J_0 = K_0 = 1$
 $J_1 = K_1 = Q_0$
 $J_2 = K_2 = Q_1 * Q_0$

Q2Q1 \ Q0	0	1
00	X	X
01	X	X
11	0	1
10	0	0


K2 map

Q2Q1 \ Q0	0	1
00	X	X
01	0	1
11	0	1
10	X	X

K1 map

Q2Q1 \ Q0	0	1
00	X	1
01	X	1
11	X	1
10	X	1

K0 map

 

Output State Transitions				Flip-flop inputs		
Present State Q2 Q1 Q0			Next State Q2 Q1 Q0			T2 T1 T0
0	0	0	0	0	1	0 0 1
0	0	1	0	1	0	0 1 1
0	1	0	0	1	1	0 0 1
0	1	1	1	0	0	1 1 1
1	0	0	1	0	1	0 0 1
1	0	1	1	1	0	0 1 1
1	1	0	1	1	1	0 0 1
1	1	1	0	0	0	1 1 1

Q2\Q1 \ Q0	0	1
00	0	0
01	0	1
11	0	1
10	0	0


T2 map

Q2\Q1 \ Q0	0	1
00	0	1
01	0	1
11	0	1
10	0	1

T1 map

Q2\Q1 \ Q0	0	1
00	1	1
01	1	1
11	1	1
10	1	1

T0 map

 

$$T0 = 1;$$

$$T1 = Q0;$$

$$T2 = Q1 * Q0$$

- JK karakteristik tablosu kullanılarak *her bir* flip-flop'un girişleri bulunur. (şimdiki ve gelecek durumlara bakarak)

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Şimdiki durum		Giriş X	Gelecek durum		Flip flop girişleri				Çıkış Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1

- Karnaugh diyagramı yardımıyla dört flip-flop'un her biri için girişlere ve çıkışa ait denklemler bulunur.
- Bu denklemler şimdiki durum ve girişler cinsindedir.
- JK FF kullanmanın avantajı: birkaç tane don't care durumuna sahip olmalarıdır. Bu sayede daha basit denklemler elde edilir.

$$J_1 = X' Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1 Q_0 X$$

$$K_1 = X + Q_0 \quad K_0 = X'$$


$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

 

- D FF karakteristik tablosu:

Q(t)	Q(t+1)	D	İşlem
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set


Şimdiki durum		Giriş	Gelecek durum		Flip flop girişleri		Çıkış
Q ₁	Q ₀	X	Q ₁	Q ₀	D ₁	D ₀	Z
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1

Karnaugh diyagramı yardımıyla aynı denklemleri bulabiliriz:

$$D_1 = Q_1 Q_0' X' + Q_1' Q_0 X'$$

$$D_0 = X + Q_1 Q_0'$$

$$Z = Q_1 Q_0 X$$

 


Analysis of Sequential Circuits.


1. Derive a) excitation equations, b) next state equations,

c) a state/output table, and

d) a state diagram

 


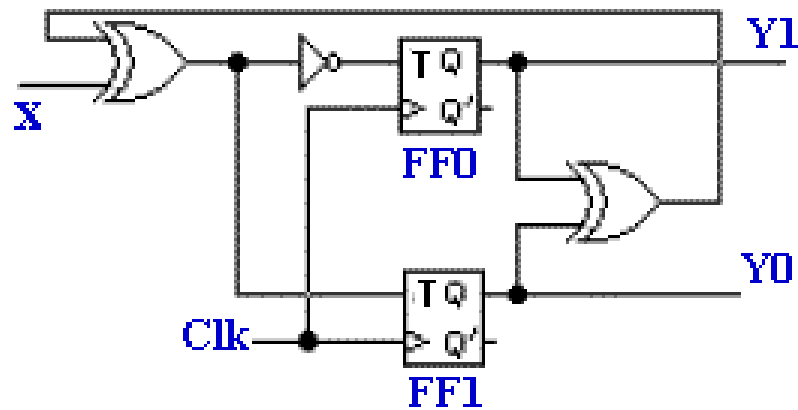2. Derive a) excitation equations, b) next state equations,



c) a state/output table,
and d) a state diagram

 3. Derive a) excitation equations, b) next state equations,



c) a state/output table,
and d) a state diagram


5. A sequential circuit uses two D flip-flops as memory elements.

The behaviour of the circuit is described by the following equations:


$$D1 = Q1 + x' * Q2$$

$$D2 = x * Q1' + x' * Q2$$


$$Z = x' * Q1 * Q2 + x * Q1' * Q2'$$

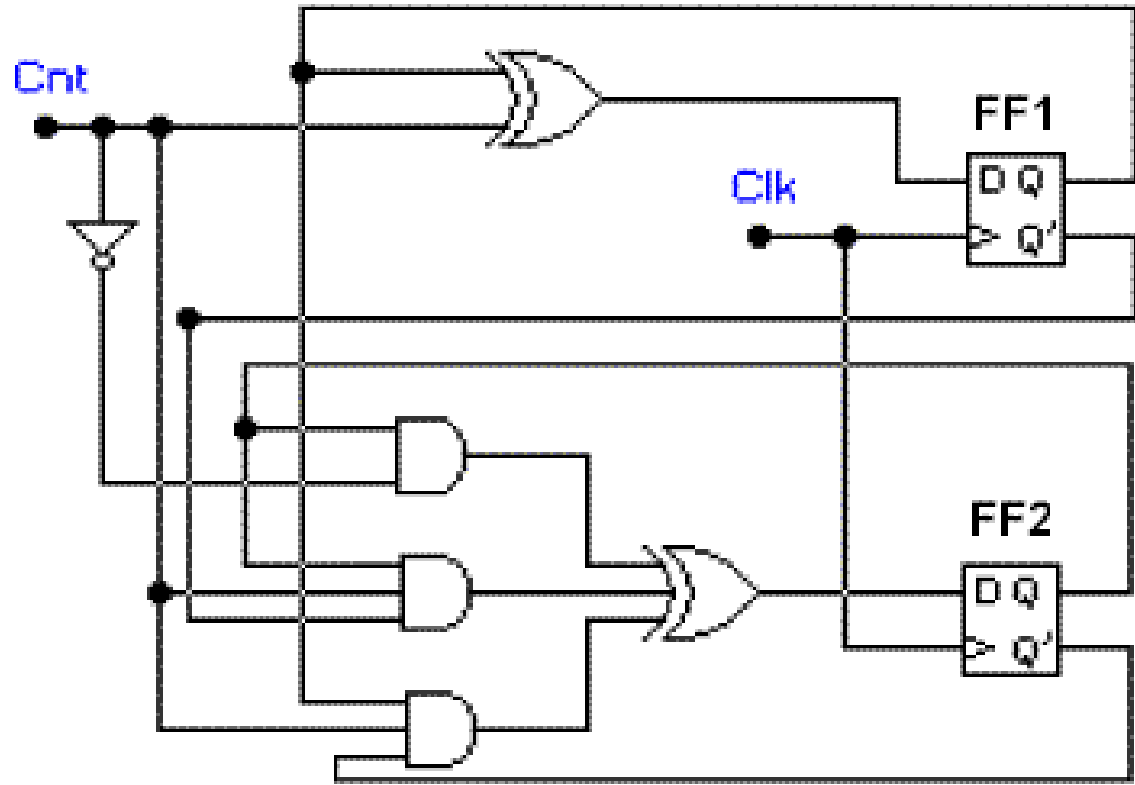

Example

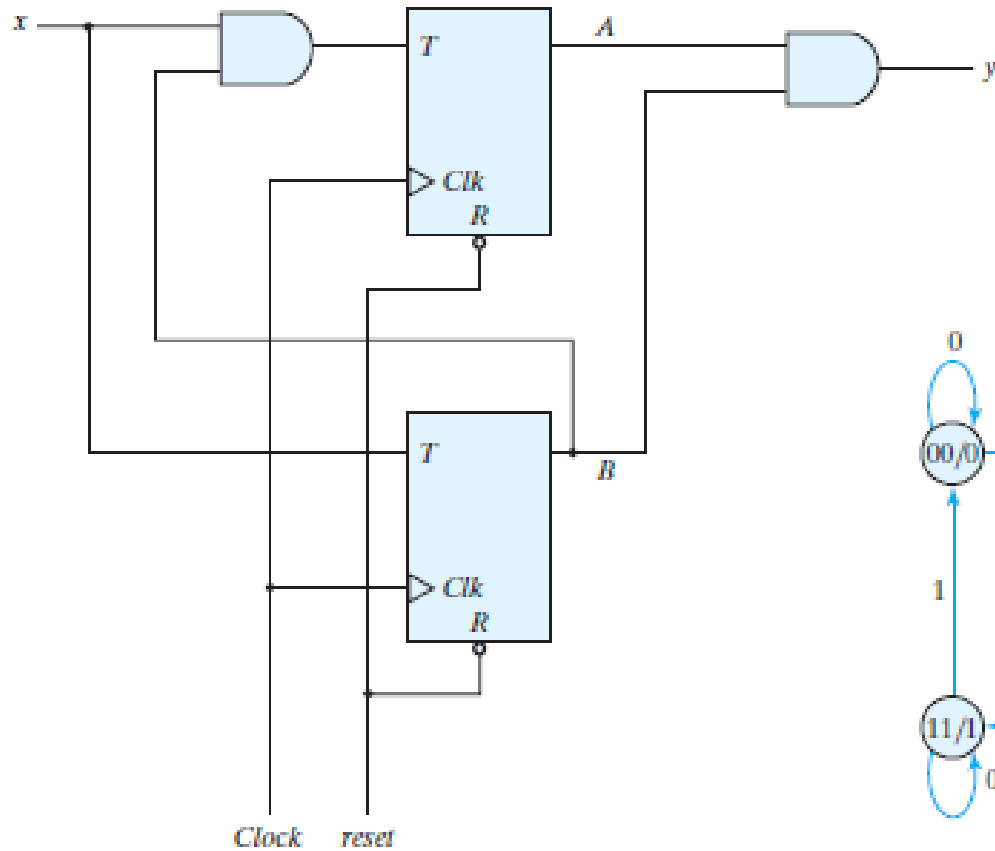

(a) Circuit diagram

 


(b) State diagram

State Table for Sequential Circuit with T Flip-Flops


Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

Example

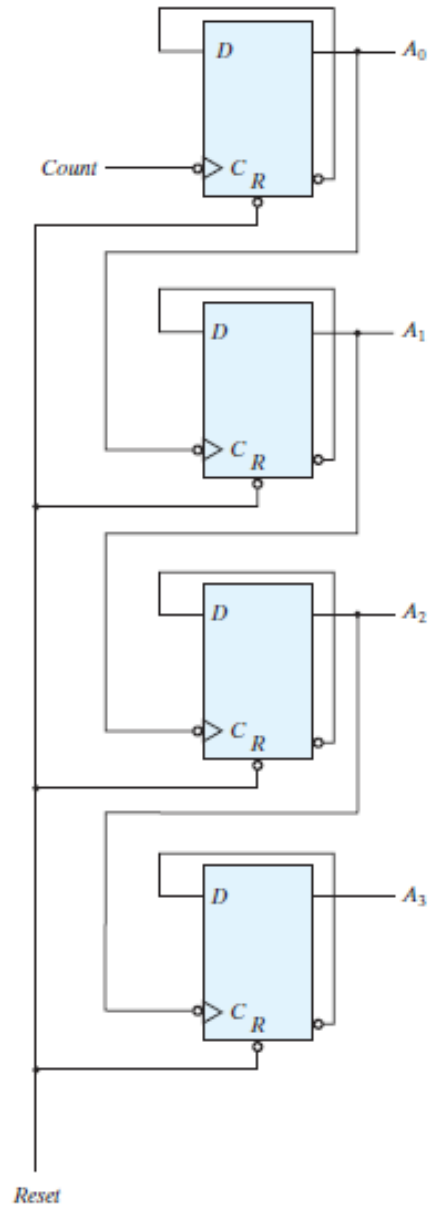


(b) With D flip-flops

Example

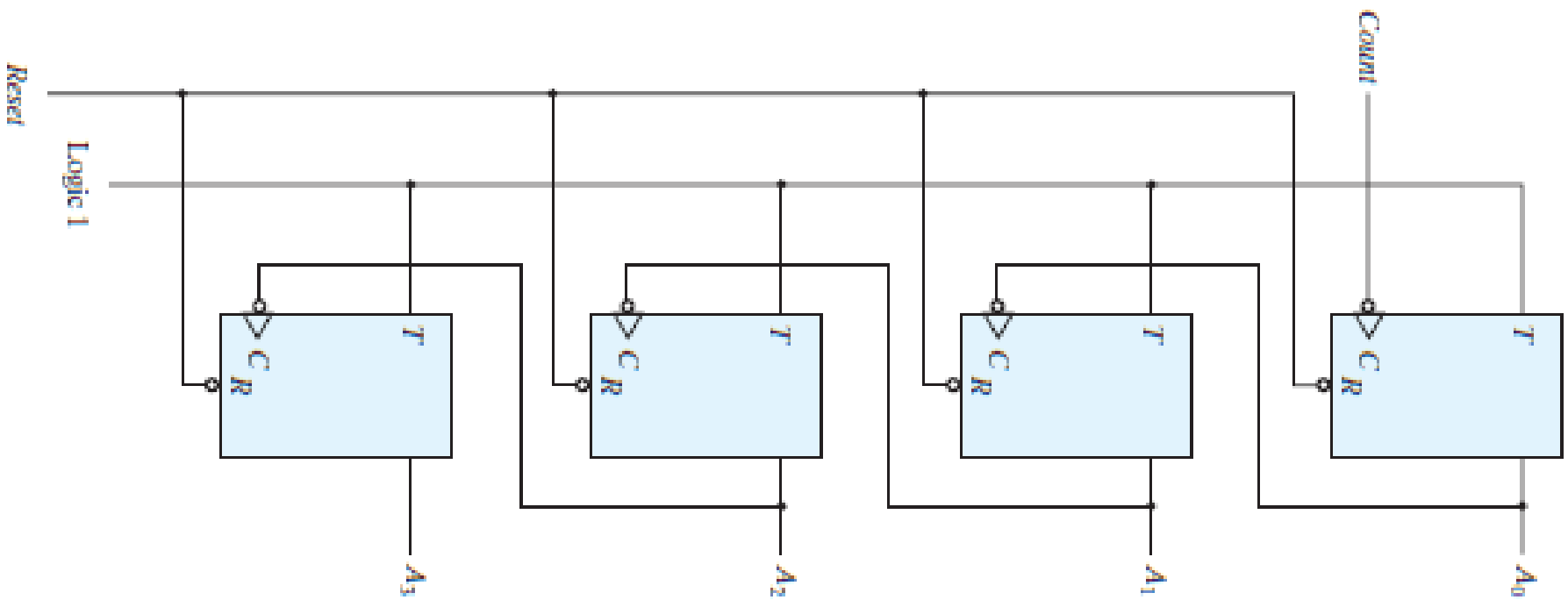


(a) With T flip-flops


Example

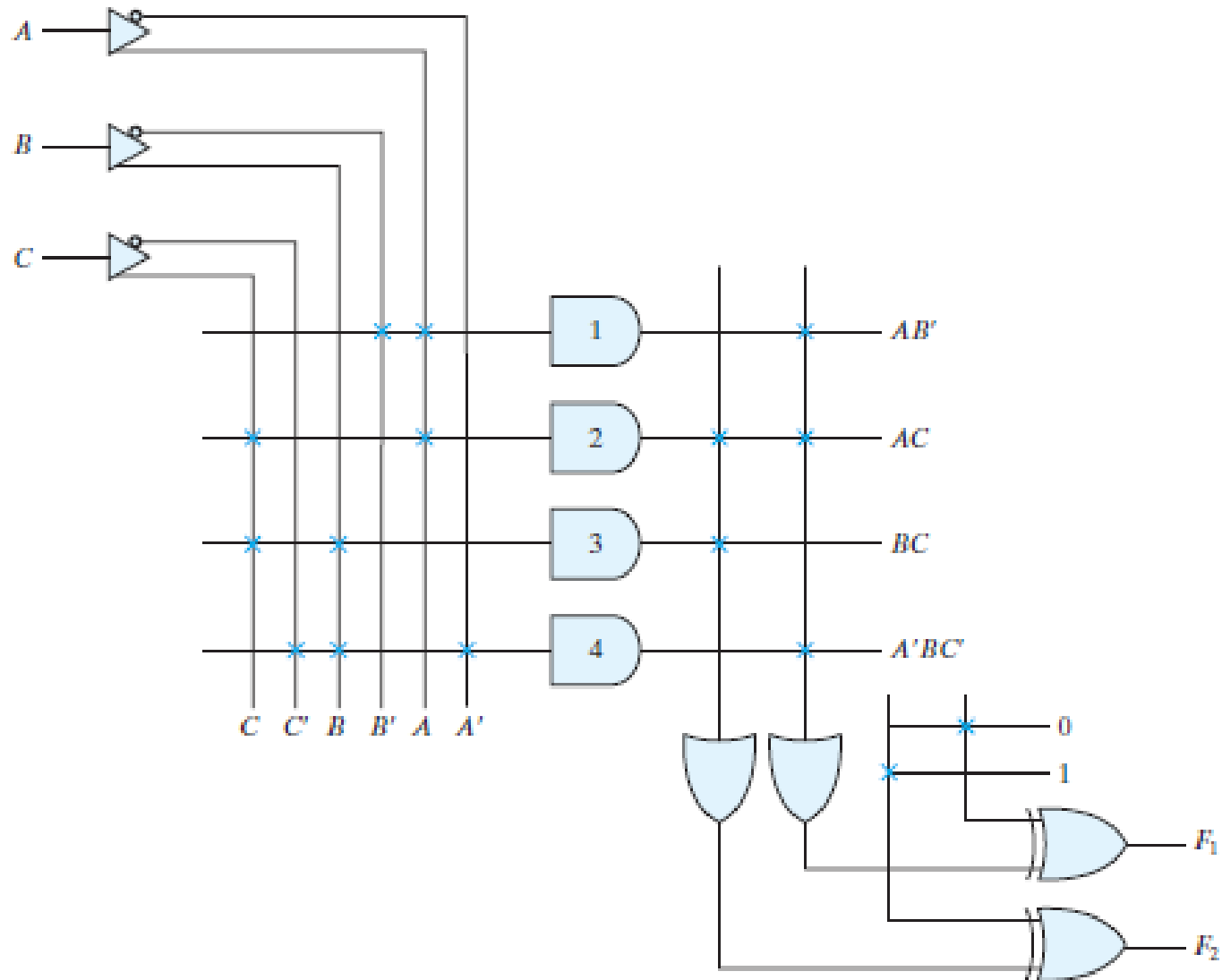


Example

 


Example

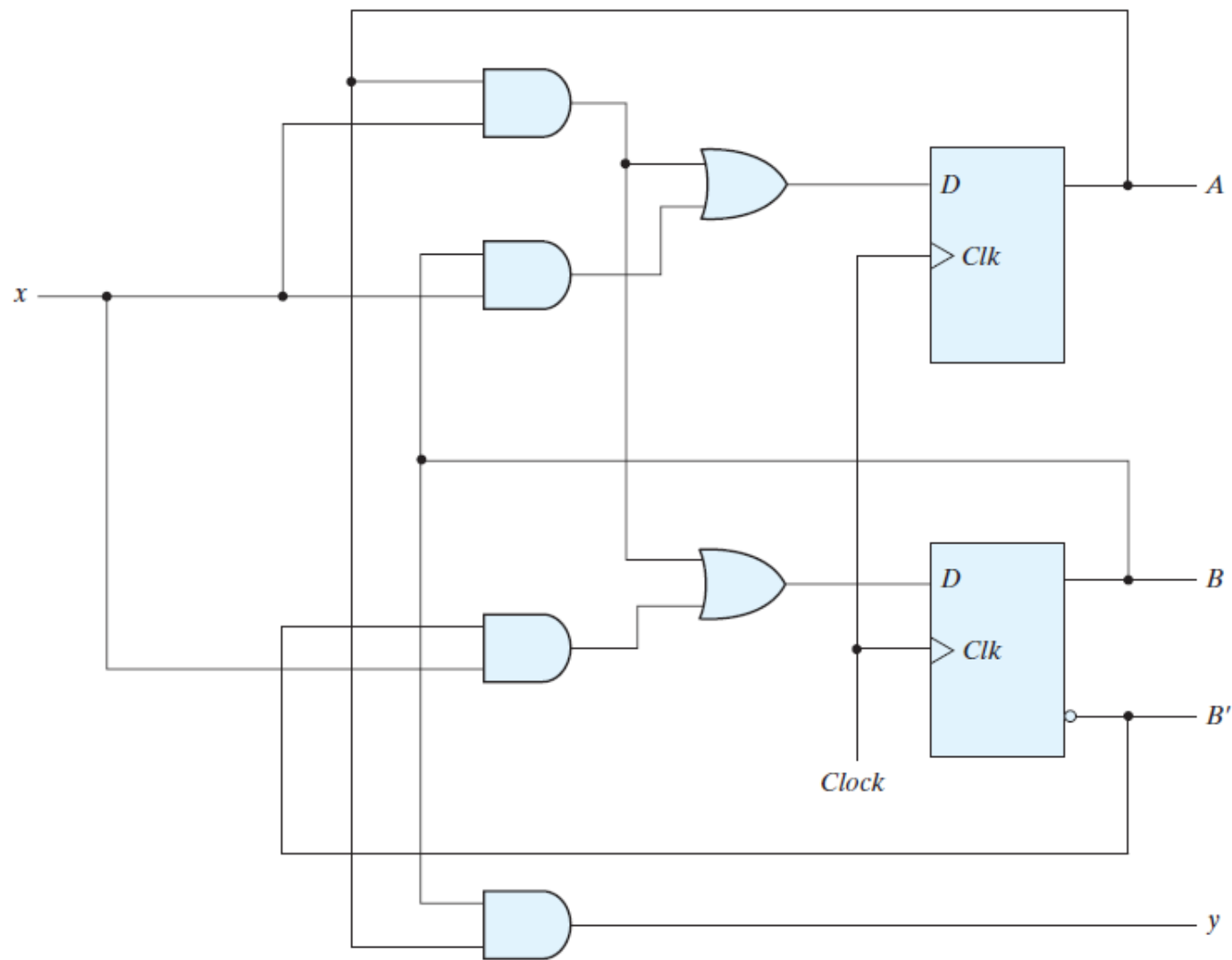


Example

 

$$D_A = Ax + Bx$$

 

$$D_B = Ax + B'x$$

 

$$y = AB$$

State Table for Sequence Detector

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Kaynakça

- <https://ocw.mit.edu/courses/electrical-engineering-and-computer-science/6-111-introductory-digital-systems-laboratory-spring-2006/lecture-notes/>
- <http://web.ee.nchu.edu.tw/~cpfan/FY92b-digital/Chapter-4.ppt>
- <http://www.cs.nccu.edu.tw/~whliao/ds2003/ds4.ppt>
- http://www.just.edu.jo/~tawalbeh/cpe252/slides/CH1_2.ppt
- Lessons In Electric Circuits, Volume IV { Digital By Tony R. Kuphaldt Fourth Edition, last update July 30, 2004.
- Digital Electronics Part I – Combinational and Sequential Logic Dr. I. J. Wassell.
- Digital Design With an Introduction to the Verilog HDL, M. Morris Mano Emeritus Professor of Computer Engineering California State University, Los Angeles; Michael D. Ciletti Emeritus Professor of Electrical and Computer Engineering University of Colorado at Colorado Springs.
- Digital Logic Design Basics, Combinational Circuits, Sequential Circuits, Pu-Jen Cheng.