### **Microwave Circuits and Antenna Design**

# **Two-Port Amplifier Design Using S-parameters**

Dr. Cahit Karakuş

2019

# **Amplifier Design using S-parameters**

- Two-Port Power Gain
- Stability
- Unilateral Gain
- CONSTANT GAIN CIRCLES

### **Two-Port Power Gain**

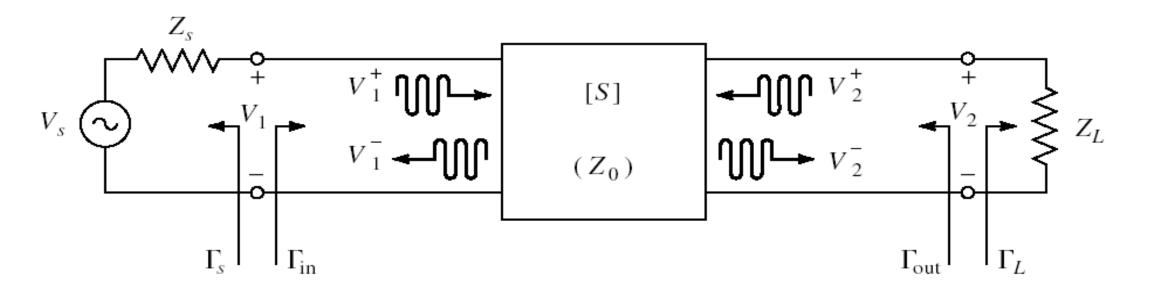


Figure 7.1: A two port network with general source and load impedance.

*Power Gain* =  $G = P_L / P_{in}$  is the ratio of power dissipated in the load  $Z_L$  to the power delivered to the input of the two-port network. This gain is independent of  $Z_s$  although some active circuits are strongly dependent on  $Z_s$ .

Available Gain =  $G_A = P_{avn} / P_{avs}$  is the ratio of the power available from the two-port network to the power available from the source. This assumes conjugate matching in both the source and the load, and depends on  $Z_S$  but not  $Z_L$ .

*Transducer Power Gain* =  $G_T = P_L / P_{avs}$  is the ratio of the power delivered to the load to the power available from the source. This depends on both  $Z_S$  and  $Z_L$ .

If the input and output are both conjugately matched to the two-port, then the gain is maximized and  $G = G_A = G_T$ 

From the definition of S parameters:

$$V_1^- = S_{11}V_1^+ + S_{12}V_2^+ = S_{11}V_1^+ + S_{12}\Gamma_L V_2^-$$
[3.1a]

$$V_2^- = S_{21}V_1^+ + S_{22}V_2^+ = S_{21}V_1^+ + S_{22}\Gamma_L V_2^-$$
[3.1b]

Eliminating  $V_2^-$  from [3.1a]:

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$
[3.2]

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = \frac{Z_{out} - Z_0}{Z_{out} + Z_0}$$
[3.3]

By voltage division:

$$V_{1} = V_{S} \frac{Z_{in}}{Z_{S} + Z_{in}} = V_{1}^{+} + V_{1}^{-} = V_{1}^{+} (1 + \Gamma_{in})$$
[3.4]

Using:

$$Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}$$
[3.5]

Solving for  $V_1^+$ :

$$V_{1}^{+} = \frac{V_{S}}{2} \frac{(1 - \Gamma_{S})}{(1 - \Gamma_{S} \Gamma_{in})}$$
[3.6]

The average power delivered to the network:

$$P_{in} = \frac{1}{2Z_0} \left| V_1^+ \left| \left( 1 - \left| \Gamma_{in} \right|^2 \right) \right| = \frac{\left| V_S \right|^2}{8Z_0} \frac{\left| 1 - \Gamma_S \right|^2}{\left| 1 - \Gamma_S \Gamma_{in} \right|^2} \left( 1 - \left| \Gamma_{in} \right|^2 \right)$$
[3.7]

The power delivered to the load is:

$$P_{L} = \frac{\left|V_{2}^{-}\right|^{2}}{2Z_{0}} \left(1 - \left|\Gamma_{L}\right|^{2}\right)$$
[3.8]

$$P_{L} = \frac{\left|V_{1}^{+}\right|^{2}}{2Z_{0}} \frac{\left|S_{21}\right|^{2} \left(1 - \left|\Gamma_{L}\right|^{2}\right)}{\left|1 - S_{22}\Gamma_{L}\right|^{2}} = \frac{\left|V_{S}\right|^{2}}{8Z_{0}} \frac{\left|S_{21}\right|^{2} \left(1 - \left|\Gamma_{L}\right|^{2}\right) 1 - \left|\Gamma_{S}\right|^{2}}{\left|1 - S_{22}\Gamma_{L}\right|^{2} \left|1 - \left|\Gamma_{S}\Gamma_{in}\right|^{2}}$$

$$(3.9)$$

The power gain can be expressed as:

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) (1 - S_{22} \Gamma_L|^2)}$$
[3.10]

The available power from the source:

$$P_{avs} = P_{in} \Big|_{\Gamma_{in} = \Gamma_{s}^{*}} = \frac{\left|V_{s}\right|^{2}}{8Z_{0}} \frac{\left|1 - \Gamma_{s}\right|^{2}}{\left(1 - \left|\Gamma_{s}\right|^{2}\right)}$$
[3.11]

The available power from the network:

$$P_{avn} = P_L \Big|_{\Gamma_L = \Gamma_{out}^*} = \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_{out}|^2) (1 - \Gamma_s)^2}{|1 - S_{22} \Gamma_{out}^*|^2 (1 - \Gamma_s \Gamma_{in})^2} \Big|_{\Gamma_L = \Gamma_{out}^*}$$
(3.12)

The power available from the network:

$$P_{avn} = \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 |1 - \Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2 (1 - |\Gamma_{out}|^2)}$$
[3.13]


The available power gain:


$$G_{A} = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^{2} (1 - |\Gamma_{s}|^{2})}{(1 - |\Gamma_{out}|^{2}) (1 - S_{11} \Gamma_{s})^{2}}$$
[3.14]

The transducer power gain:

$$G_{T} = \frac{P_{L}}{P_{avs}} = \frac{|S_{21}|^{2} (1 - |\Gamma_{s}|^{2}) (1 - |\Gamma_{L}|^{2})}{|1 - S_{22} \Gamma_{L}|^{2} |1 - \Gamma_{s} \Gamma_{in}|^{2}}$$
[3.15]

#### **AMPLIFIER BLOCK DIAGRAM**

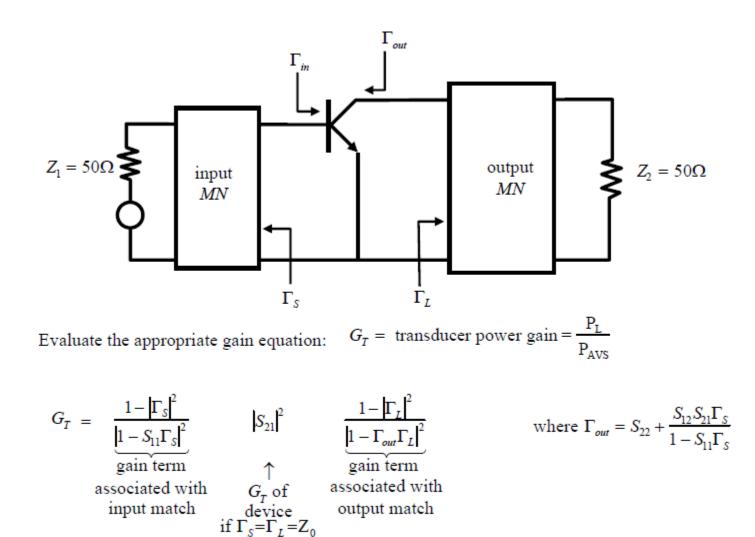


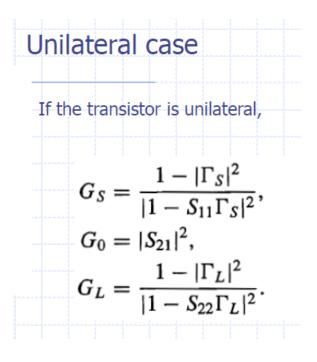


So, if you are given the S params and  $\Gamma_S, \Gamma_L$  then you can calculate the gain.

Note however that  $\Gamma_{out}$  depends on  $\Gamma_S$  unless  $S_{12} = 0!$ 
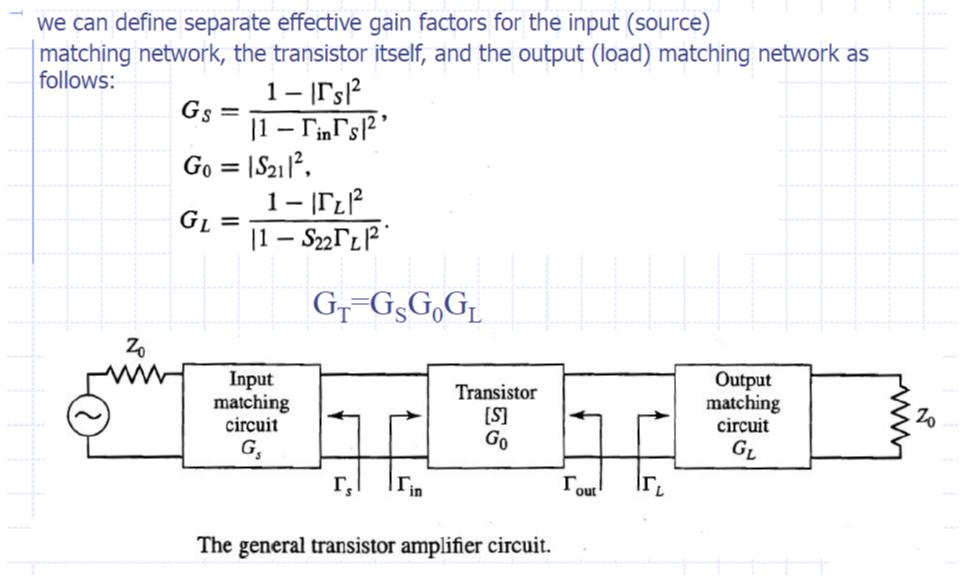
### Further discussion of two-ports power gains



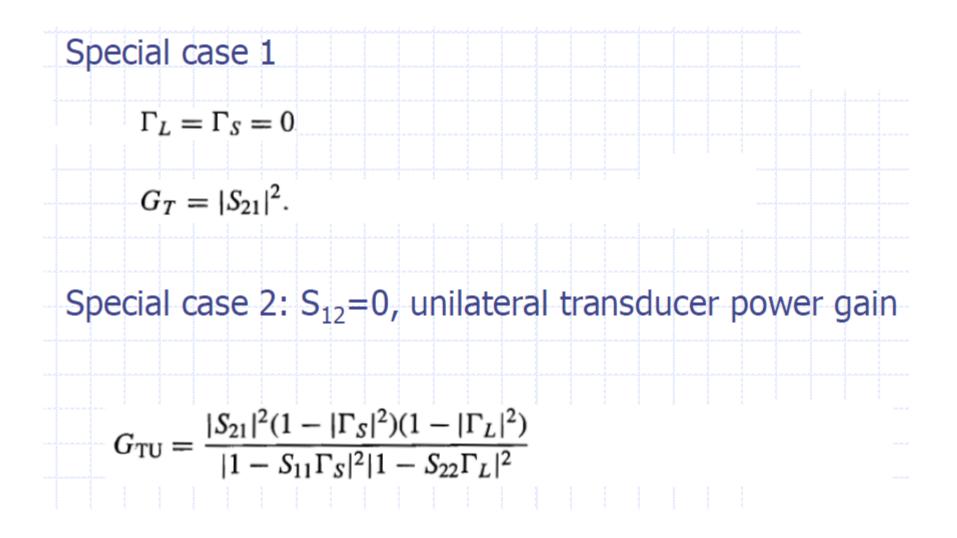

#### EXAMPLE COMPARISON OF POWER GAIN DEFINITIONS

A microwave transistor has the following S parameters at 10 GHz, with a 50  $\Omega$  reference impedance:

 $S_{11} = 0.45 \angle 150^{\circ}$   $S_{12} = 0.01 \angle -10^{\circ}$   $S_{21} = 2.05 \angle 10^{\circ}$  $S_{22} = 0.40 \angle -150^{\circ}$ 

The source impedance is  $Z_s = 20 \ \Omega$  and the load impedance is  $Z_L = 30 \ \Omega$ . Compute the power gain, the available gain, and the transducer power gain.

#### Solution

From (6.4a,b) the reflection coefficients at the source and load are

$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} = \frac{20 - 50}{20 + 50} = -0.429,$$
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - 50}{30 + 50} = -0.250.$$

the reflection coefficients seen looking at the input and output of the terminated network are

$$\begin{split} \Gamma_{\rm in} &= S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \\ &= 0.45\angle 150^\circ + \frac{(0.01\angle -10^\circ)(2.05\angle 10^\circ)(-0.250)}{1 - (0.40\angle -150^\circ)(-0.250)} = 0.455\angle 150^\circ, \\ \Gamma_{\rm out} &= S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \\ &= 0.40\angle -150^\circ + \frac{(0.01\angle -10^\circ)(2.05\angle 10^\circ)(-0.429)}{1 - (0.45\angle 150^\circ)(-0.429)} = 0.408\angle -151^\circ. \end{split}$$

the power gain is

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{\text{in}}|^2)|1 - S_{22}\Gamma_L|^2}$$
  
= 
$$\frac{(2.05)^2 [1 - (0.250)^2]}{|1 - (0.402 - 150^\circ)(-0.250)|^2 [1 - (0.455)^2]} = 5.94.$$

the available power gain is

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|1 - S_{11} \Gamma_S|^2 (1 - |\Gamma_{out}|^2)}$$
$$= \frac{(2.05)^2 [1 - (0.429)^2]}{|1 - (0.45 \angle 150^\circ) (-0.429)|^2 [1 - (0.408)^2]} = 5.85.$$

the transducer power gain is


$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2}$$
  
= 
$$\frac{(2.05)^2 [1 - (0.429)^2] [1 - (0.250)^2]}{|1 - (0.402 - 150^\circ) (-0.250)|^2 |1 - (-0.429) (0.4552 150^\circ)|^2} = 5.49$$

## Örnek:

2GHz amplifier 
$$(Z_o = 50 \Omega)$$
 with  $S_{11} = 0.97 \angle -43^\circ$ ,  $S_{12} = 0$ ,  
 $S_{21} = 3.39 \angle 140^\circ$ ,  $S_{22} = 0.63 \angle -32^\circ$ ,  $\Gamma_s = 0.97 \angle 43^\circ$ ,  $\Gamma_L = 0.63 \angle 32^\circ$ ,  
 $\rightarrow G_T, G_P, G_A$   
 $S_{12} = 0 \rightarrow \Gamma_m = S_{11}, \Gamma_{out} = S_{22}$   
 $\Gamma_s = S_{11}^*, \Gamma_L = S_{22}^*$   
 $G_P = \frac{P_L}{P_m} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_m|^2)|1 - S_{22}\Gamma_L|^2}, G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{(1 - |\Gamma_{out}|^2)|1 - S_{11}\Gamma_s|^2}$   
 $G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_m|^2 |1 - S_{22}\Gamma_L|^2}$   
 $G_T = G_A = G_P = G_{TU \max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} = 322.42 = 25 dB$ 
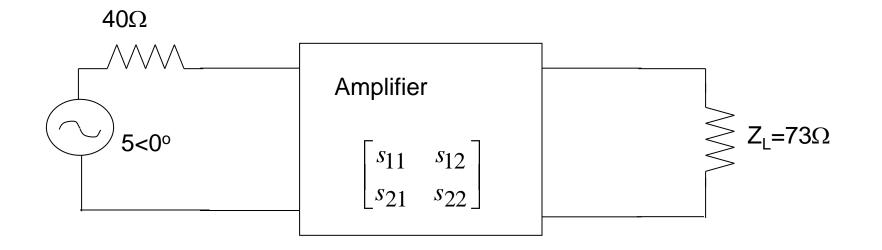
### **Example:** Gain Expressions

- An RF amplifier has the following S-parameters at f<sub>o</sub>: s<sub>11</sub>=0.3<-70°, s<sub>21</sub>=3.5<85°, s<sub>12</sub>=0.2<-10°, s<sub>22</sub>=0.4<-45°. The system is shown below. Assuming reference impedance (used for measuring the S-parameters) Z<sub>o</sub>=50Ω, find:
- (a) G<sub>T</sub>, G<sub>A</sub>, G<sub>P</sub>.
- (b) P<sub>L</sub>, P<sub>A</sub>, P<sub>inc</sub>.



## Example Cont...

- Step 1 Find  $\Gamma_s$  and  $\Gamma_L$ .
- Step 2 Find  $\Gamma_1$  and  $\Gamma_2$ .
- Step 3 Find G,  $G_A$ ,  $G_T$ .
- Step 4 Find  $P_L$ ,  $P_A$ .
- D=s11s22-s12s21

• Gp=GT  

$$P_A = \frac{|V_s|^2}{8 \cdot \text{Re}[Z_s]} = 0.078W$$
Try to derive  
These 2 relations  
 $P_{in} = P_A \left( 1 - \left| \frac{Z_1 - Z_s}{Z_1 + Z_s} \cdot Z_o \right|^2 \right) = 0.0714W$ 

$$P_L = G_P P_{in} = 0.9814W$$

Note that this is an analysis problem.

$$\Gamma_{s} = \frac{Z_{s} - Z_{o}}{Z_{s} + Z_{o}} = -0.111 \qquad \Gamma_{L} = \frac{Z_{L} - Z_{o}}{Z_{L} + Z_{o}} = 0.187$$
$$\Gamma_{1} = \frac{s_{11} - D\Gamma_{L}}{1 - s_{22}\Gamma_{L}} = 0.146 - j0.151$$
$$\Gamma_{2} = \frac{s_{22} - D\Gamma_{s}}{1 - s_{11}\Gamma_{s}} = 0.265 - j0.358$$

$$G = \frac{|s_{21}|^{2} (1 - |\Gamma_{L}|^{2})}{|1 - s_{22} \Gamma_{L}|^{2} (1 - |\Gamma_{L}|^{2})} = 13.742$$

$$G_{A} = \frac{\left(1 - |\Gamma_{s}|^{2}\right)|s_{21}|^{2}}{|1 - s_{11}\Gamma_{s}|^{2}\left(1 - |\Gamma_{2}|^{2}\right)} = 14.739$$


$$G_{T} = \frac{\left(1 - |\Gamma_{L}|^{2}\right)|s_{21}|^{2}\left(1 - |\Gamma_{s}|^{2}\right)}{|1 - s_{22}\Gamma_{L}|^{2}|1 - \Gamma_{1}\Gamma_{s}|^{2}} = 12.562$$




Oscillation is possible if either the input or output port impedance has a negative real part; this would then imply that  $|\Gamma_{in}| > 1$  or  $|\Gamma_{out}| > 1$ .

Because  $\Gamma_{in}$  and  $\Gamma_{out}$  depend on the

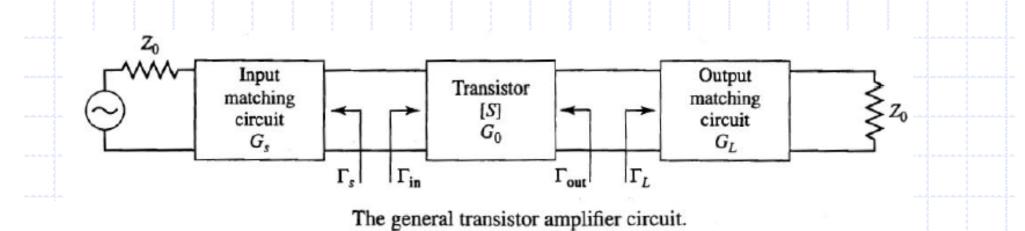source and load matching networks, the stability of the amplifier depends on  $\Gamma_S$  and  $\Gamma_L$ 



- Unconditional stability: The network is unconditionally stable if  $|\Gamma_{in}| < 1$  and  $|\Gamma_{out}| < 1$  for all passive source and load impedances (i.e.,  $|\Gamma_S| < 1$  and  $|\Gamma_L| < 1$ ).
- Conditional stability: The network is conditionally stable if  $|\Gamma_{in}| < 1$  and  $|\Gamma_{out}| < 1$
- only for a certain range of passive source and load impedances. This case is also referred to as *potentially unstable*.

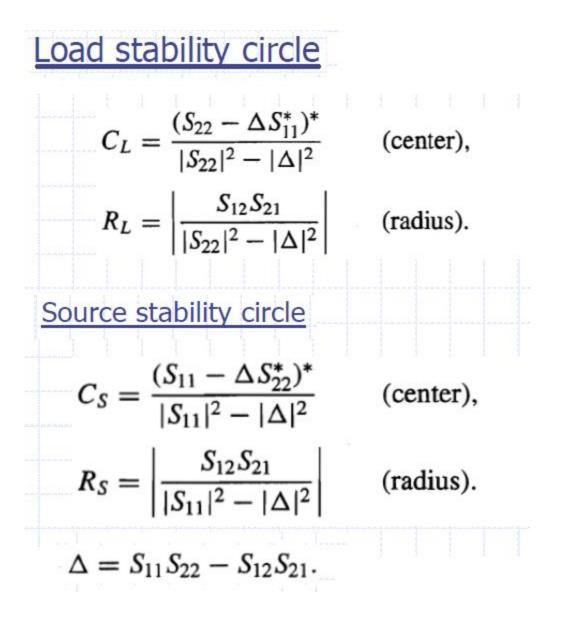

#### Unconditional stable:

If the device is unconditionally stable, the stability circles must be completely outside (or totally enclose) the Smith chart.

 $||C_L| - R_L| > 1,$  for  $|S_{11}| < 1,$  $||C_S| - R_S| > 1,$  for  $|S_{22}| < 1.$ 

If  $|S_{11}| > 1$  or  $|S_{22}| > 1$ , the amplifier cannot be unconditionally stable because we can always have a source or load impedance of  $Z_0$  leading to  $\Gamma_S = 0$  or  $\Gamma_L = 0$ , thus causing  $|\Gamma_{in}| > 1$  or  $|\Gamma_{out}| > 1$ . If the device is only conditionally stable, operating points for  $\Gamma_S$ and  $\Gamma_L$  must be chosen in stable regions, and it is good practice to check the stability at several frequencies near the design frequency. If it is possible to accept a design with less than maximum gain, a transistor can usually be made to be unconditionally stable by using resistive loading.

#### Tests for unconditional stability

#### $\textbf{K-}\Delta \, \textbf{test}$

These two conditions are necessary and sufficient for unconditional stability, and are easily evaluated.

$$\longrightarrow K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} > 1,$$

$$\implies |\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1,$$

recall from the previous paragraph that we must have  $|S_{11}| < 1$  and  $|S_{22}| < 1$  if the device is to be unconditionally stable.

While the  $K-\Delta$  test is a mathematically rigorous condition for unconditional stability, it cannot be used to compare the relative stability of two or more devices since it involves constraints on two separate parameters. Recently, however, a new criterion has been proposed that combines the S parameters in a test involving only a single parameter,  $\mu$ , defined as

A quantitative test  
$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}^*| + |S_{12}S_{21}|} > 1.$$

Thus, if  $\mu > 1$ , the device is unconditionally stable. In addition, larger values of  $\mu$  imply greater stability.

$$\Gamma_{\text{out}} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = \frac{S_{22} - \Delta\Gamma_S}{1 - S_{11}\Gamma_S},$$
  
Unconditional stability implie that  $|\Gamma_{\text{out}}| < 1$  for any passive source termination,  $\Gamma_S$ .

The S parameters for the HP HFET-102 GaAs FET at 2 GHz with a bias voltage of Vgs = 0 are given as follow (Z<sub>0</sub> = 50 Ohm):

$$\begin{split} \mathbf{S}_{11} &= 0.894 < -60.6\\ \mathbf{S}_{21} &= 3.122 < 123.6\\ \mathbf{S}_{12} &= 0.020 < 62.4\\ \mathbf{S}_{22} &= 0.781 < -27.6 \end{split}$$

Determine the stability of this transistor using the K- $\Delta$  test and the  $\mu$  test, and plot the stability circles on the Smith Chart

Remember, criteria for unconditional stability is: For the K- $\Delta$  test:

$$\left|\Delta\right| = \left|S_{11}S_{22} - S_{12}S_{21}\right| < 1$$
$$K = \frac{1 - \left|S_{11}\right|^2 - \left|S_{22}\right|^2 + \left|\Delta\right|^2}{2\left|S_{12}S_{21}\right|} > 1$$

For the  $\mu$  test:

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}^*| + |S_{12}S_{21}|} > 1$$

Calculation results:

For the *K*- $\Delta$  test:

$$|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| = 0.696 < 1$$
$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} = 0.607 < 1$$

For the  $\mu$  test:

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}^*| + |S_{12}S_{21}|} = 0.86 < 1$$

Which indicates potential instability

Calculation for the input and output stability circles:

Output stability circle center and radius:

$$C_{L} = \frac{\left(S_{22} - \Delta S_{11}^{*}\right)^{*}}{\left|S_{22}\right|^{2} - \left|\Delta\right|^{2}} = 1.361 < 47$$
$$R_{L} = \left|\frac{S_{12}S_{21}}{\left|S_{22}\right|^{2} - \left|\Delta\right|^{2}}\right| = 0.50$$

Input stability circle and radius

$$C_{s} = \frac{\left(S_{11} - \Delta S_{22}^{*}\right)^{*}}{\left|S_{11}\right|^{2} - \left|\Delta\right|^{2}} = 1.132 < 68$$
$$R_{s} = \left|\frac{S_{12}S_{21}}{\left|S_{11}\right|^{2} - \left|\Delta\right|^{2}}\right| = 0.199$$

### STABILITY

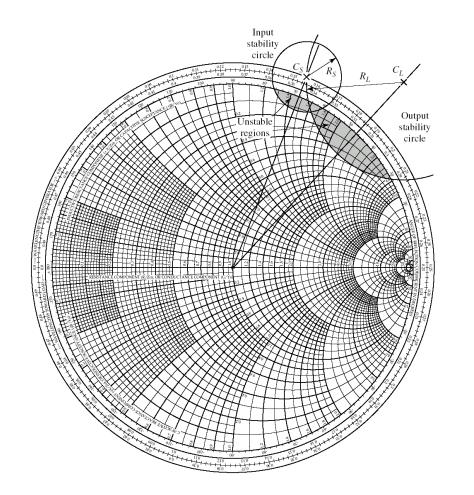


Figure 7.4: Example of stability circles

# A unilateral device condition for unconditional stability

 For a unilateral device condition for unconditional stability in terms of S parameters is |S<sub>11</sub>|<1, |S<sub>22</sub>|<1.</li>

Explanation: For a unilateral device, the condition for unconditional stability is  $|S_{11}| < 1$ ,  $|S_{22}| < 1$ .  $S_{11}$  parameter signifies the amount of power reflected back to port 1, which is the input port of the transistor. If this S parameter is greater is than 1, more amount of power is reflected back implying the amplifier is unstable.

If |S<sub>11</sub>|>1 or |S<sub>22</sub>|>1, the amplifier cannot be unconditionally stable.
 If |S<sub>11</sub>|>1 or |S<sub>22</sub>|>1, the amplifier cannot be unconditionally stable because we can have a source or load impedance of Z<sub>o</sub> leading to Γs=0 or ΓL=0, thus causing output and input reflection coefficients greater than 1.

# Condition for unconditional stability

- The condition for unconditional stability of a transistor is |Δ| < 1 and K>1. Here, |Δ| and K are defined in terms of the s parameters of the transistor by defining the S matrix. To determine the unconditional stability of a transistor in K-Δ method, the S matrix of the transistor must be known.
- If the S parameters of a transistor given are S<sub>11</sub>=-0.811-j0.311 S<sub>12</sub>= 0.0306+j0.0048 S<sub>21</sub>=2.06+j3.717 S<sub>22</sub>=-0.230-j0.4517

Then  $\Delta$  for the given transistor is 0.336.

Explanation: Given the S parameters of a transistor, the  $\Delta$  value of the transistor is given by  $|S_{11}S_{22}-S_{12}S_{21}|$ . Substituting the given values in the above equation, the  $\Delta$  of the transistor is 0.336.

### **Unilateral Gain**

#### **Unilateral Gain**

This time the mismatch factors,  $G_S$  and  $G_L$ , are independent of each other, meaning that the input and output ports of the device can be matched independently.  $G_S$  and  $G_L$ result from (13) and (14) when we set  $\Gamma_{in} = S_{11}$  and  $\Gamma_{out} = S_{22}$ .  $G_o$  simply represents the transducer gain of the active device when terminated in the system characteristic impedance,  $Z_o$ .

It is a simple matter to show that, for a unilateral device, maximum gain is obtained when we set:

$$\Gamma_S = S_{11}^*$$

and

$$\Gamma_L = S_{22}^*$$

(17) then gives the value of the maximum unilateral gain as:

$$G_{TU_{max}} = \frac{1}{|1 - |S_{11}|^2|} |S_{21}|^2 \frac{1}{|1 - |S_{22}|^2|}$$


A further useful consequence of assuming unilaterality is that Rollett's stability factor tends to infinity and the stability criteria (??) simply reduce to:

 $|S_{11}| < 1$  $|S_{22}| < 1$ 

### **Amplifier Design using S-parameters**
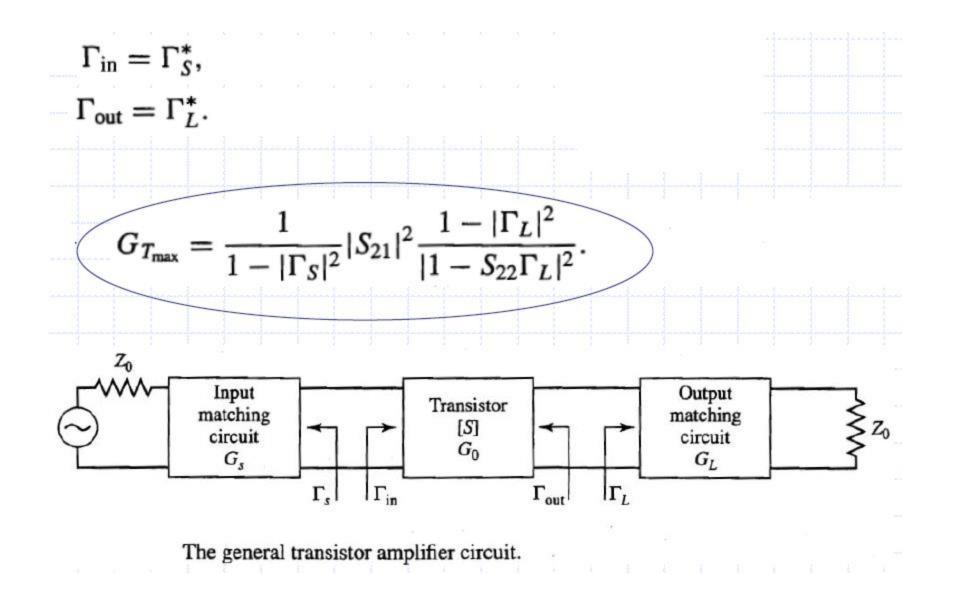
# **Amplifier Design using S-parameters**

- Stability check
- Matching network design according to gain, power or noise maximization
- Conjugate match for maximum gain but usually lower bandwidth.
- Trade off between gain and bandwidth



In the general case with a bilateral transistor  $(|S_{12}| \neq 0)$ ,  $\Gamma_{in}$  is affected by  $\Gamma_{out}$ , and vice versa, so that the input and output sections must be matched simultaneously. the necessary equations:

$$\begin{split} (S_{11} - \Delta S_{22}^*)\Gamma_S^2 + (|\Delta|^2 - |S_{11}|^2 + |S_{22}|^2 - 1)\Gamma_S + (S_{11}^* - \Delta^* S_{22}) &= 0. \\ \Gamma_S &= \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}. \\ \Gamma_L &= \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}. \\ B_1 &= 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta^2|, \\ B_2 &= 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta^2|, \\ C_1 &= S_{11} - \Delta S_{22}^*, \\ C_2 &= S_{22} - \Delta S_{11}^*. \end{split}$$

#### Solutions to

 $\Gamma_s$  and  $\Gamma_L$  are only possible if the quantity within the square root is positive, and it can be shown that this is equivalent to requiring K > 1.

Thus unconditionally stable devices can always be conjugately matched for maximum gain, and potentially unstable devices can be conjugately matched if K > 1 and  $|\Delta| < 1$ .

for the unilateral case. When  $S_{12} = 0$ ,  $\Gamma_S = S_{11}^*$  and  $\Gamma_L = S_{22}^*$ , and then the maximum transducer gain of reduces to

$$G_{TU_{\max}} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}.$$

### Maximum stable gain

If the transistor is unconditionally stable, so that K > 1, the maximum transducer power gain of (6.40) can be simply rewritten as follows:

$$G_{T_{\text{max}}} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1}).$$

The maximum gain does not provide a meaningful result if the device is <u>only</u> <u>conditionally stable</u>, since simultaneous conjugate matching of the source and load are not possible if K < 1

In this case <u>a useful figure of merit is the maximum stable gain</u>, defined as the maximum transducer power gain of (6.46) with K = 1.

For K = 1: 
$$G_{\rm msg} = \frac{|S_{21}|}{|S_{12}|}$$

The maximum stable gain is easy to compute and offers a convenient way to compare the gain of various devices <u>under stable operating conditions</u>.

#### CONJUGATELY MATCHED AMPLIFIER DESIGN

Design an amplifier for maximum gain at 4.0 GHz using single-stub matching sections. Calculate and plot the input return loss and the gain from 3 to 5 GHz. Use a GaAs FET with the following S parameters ( $Z_0 = 50 \Omega$ ):

f (GHz)	S <sub>11</sub>	S <sub>21</sub>	S <sub>12</sub>	S <sub>22</sub>
3.0	0.80∠ <b>—</b> 89°	2.86∠99°	0. <b>0</b> 3∠56°	0.762-41°
4.0	0.72∠-116°	2.60∠76°	0.03∠57°	0.732-54°
5.0	0.66∠-142°	2.39/54°	0.03∠62°	0.72∠-68°

#### Solution

We first check for unconditional stability of the transistor by calculating  $\Delta$  and K at 4.0 GHz:

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 0.488\angle -162^{\circ},$$
  
$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} = 1.195.$$

Since  $|\Delta| < 1$  and K > 1, the transistor is unconditionally stable at 4.0 GHz. There is therefore no need to plot the stability circles. For maximum gain, we should design the matching sections for a conjugate match to the transistor. Thus,  $\Gamma_S = \Gamma_{in}^*$  and  $\Gamma_L = \Gamma_{out}^*$ , and  $\Gamma_S$  and  $\Gamma_L$  can be determined :

$$\Gamma_{S} = \frac{B_{1} \pm \sqrt{B_{1}^{2} - 4|C_{1}|^{2}}}{2C_{1}} = 0.872\angle 123^{\circ}$$
$$\Gamma_{L} = \frac{B_{2} \pm \sqrt{B_{2}^{2} - 4|C_{2}|^{2}}}{2C_{2}} = 0.876\angle 61^{\circ}.$$

Then the effective gain factors can be calculated as

$$G_{S} = \frac{1}{1 - |\Gamma_{S}|^{2}} = 4.17 = 6.20 \text{ dB},$$
  


$$G_{0} = |S_{21}|^{2} = 6.76 = 8.30 \text{ dB},$$
  

$$G_{L} = \frac{1 - |\Gamma_{L}|^{2}}{|1 - S_{22}\Gamma_{L}|^{2}} = 1.67 = 2.22 \text{ dB}.$$

So the overall transducer gain will be

$$G_{T_{\text{max}}} = 6.20 + 8.30 + 2.22 = 16.7 \text{ dB}.$$

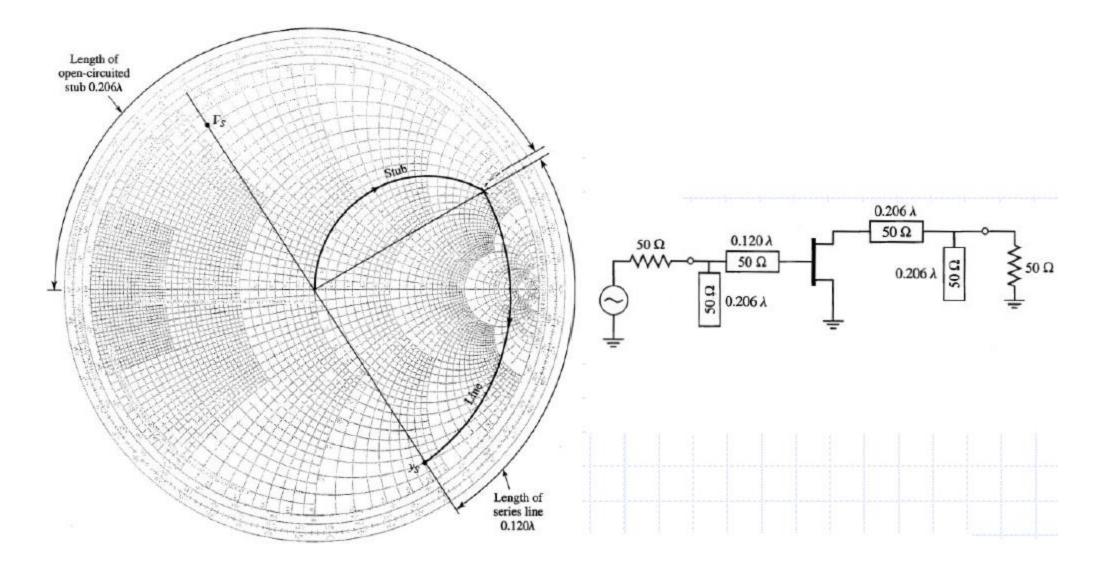The matching networks can easily be determined with a Smith chart. For the input matching section, we first plot  $\Gamma_S$ ,



# Example

Design an amplifier for a maximum gain at 4.0 GHz. Calculate the overall transducer gain, *G*, and the maximum overall transducer gain  $G_{TMAX}$ . The S parameters for the GaAs FET at 4 GHz given as follow (Z<sub>0</sub> = 50 Ohm):

$$\begin{split} \mathbf{S}_{11} &= 0.72 < -116\\ \mathbf{S}_{21} &= 2.60 < 76\\ \mathbf{S}_{12} &= 0.03 < 57\\ \mathbf{S}_{22} &= 0.73 < -68 \end{split}$$

# Example (Cont)

Determine the stability of this transistor using the K- $\Delta$  test

$$S_{11}S_{22} - S_{12}S_{21} = 0.488 < -162$$
$$|\Delta| = 0.488$$
$$1 - |S|^2 - |S|^2 + |\Delta|^2$$

$$K = \frac{1 - |S_{11}| - |S_{22}| + |\Delta|}{2|S_{12}S_{21}|} = 1.195$$

Since  $|\Delta| < 1$  and K > 1, the transistor is unconditionally stable at 4.0 GHz.

For the maximum gain, we should design the matching sections for a conjugate match to the transistor. Thus,  $\Gamma_{\rm S} = \Gamma_{\rm in}^*$  and  $\Gamma_{\rm L} = \Gamma_{\rm out}^*$ ,  $\Gamma_{\rm S}$  and  $\Gamma_{\rm L}$  can be determined from;

$$\Gamma_{s} = \frac{B_{1} \pm \sqrt{B_{2}^{2} - 4|C_{1}|^{2}}}{2C_{1}} = 0.872 < 123$$
$$\Gamma_{L} = \frac{B_{2} \pm \sqrt{B_{1}^{2} - 4|C_{2}|^{2}}}{2C_{2}} = 0.876 < 61$$

# Example

The effective gain factors can calculated as:

$$G_{s} = \frac{1}{1 - |S_{11}|^{2}} = 4.17 = 6.20dB$$
$$G_{0} = |S_{21}|^{2} = 6.76 = 8.30dB$$
$$G_{L} = \frac{1 - |\Gamma_{L}|^{2}}{|1 - S_{22}\Gamma_{L}|^{2}} = 1.67 = 2.22dB$$

So the overall maximum transducer gain will be;

$$G_{T_{\text{max}}} = 6.20 + 8.30 + 2.22 = 16.7 dB$$

# Example 4

An FET is biased for minimum noise figure, and has the following S parameters at 4 GHz:

$$\begin{split} \mathbf{S}_{11} &= 0.60 < -60\\ \mathbf{S}_{21} &= 1.90 < 81\\ \mathbf{S}_{12} &= 0.05 < 26\\ \mathbf{S}_{22} &= 0.50 < -60 \end{split}$$

For design purposes, assume the device is unilateral and calculate the max error in  $G_T$  resulting from this assumption.

# **Unilateral form**

- In many practical cases  $|S_{12}|$  is small enough to be ignored, the device then can be assumed to be unilateral, which greatly simplifies design procedure
- Error in the transducer gain caused by approximating  $|S_{12}|$  as zero is given by the ratio  $G_T/G_{TU}$ , and be bounded by:

$$\frac{1}{(1+U)^2} < \frac{G_{T}}{G_{TU}} < \frac{1}{(1-U)^2}$$

Where U is defined as the unilateral figure of merit

$$U = \frac{|S_{12}||S_{21}||S_{11}||S_{22}|}{(1-|S_{11}|^2)(1-|S_{22}|^2)}$$

To compute the unilateral figure of merit;

$$U = \frac{\left|S_{12} \|S_{21} \|S_{11} \|S_{22}\right|}{(1 - \left|S_{11}\right|^2)(1 - \left|S_{22}\right|^2)} = 0.059$$

Then the ratio of  $G_T/G_{TU}$  is bounded as;

$$\frac{1}{(1+U)^2} < \frac{G_{T}}{G_{TU}} < \frac{1}{(1-U)^2}$$

$$0.891 < \frac{G_{T}}{G_{TU}} < 1.130$$

In dB, this is;

# $-0.50 < G_{T} - G_{TU} < 0.53 dB$

Where  $G_T$  and  $G_{TU}$  are now in dB. Thus we should expect less than about  $\pm 0.5$  dB error in gain.

# **CONSTANT GAIN CIRCLES**

# Constant gain circle and design for specified gain

- In many cases it is preferable to design for less than the maximum obtainable gain, to improve bandwidth, to obtain a specific value of amplifier gain, or to minimize the effect of device variations.
- This can be done by designing the input and output matching sections to have less than maximum gains; in other words, impedance mismatches are purposely introduced to reduce the overall gain.
- The design procedure is facilitated by plotting constant gain circles on a Smith chart, to represent loci of  $\Gamma_{s \text{ and } \Gamma_{L}}$  that give fixed values of gain for the input and output sections (Gs and GL).

# Constant gain circle and design for specified gain

Only unilateral case is shown for simplicity

The error in the

transducer gain caused by approximating  $|S_{12}|$  as zero is given by the ratio  $G_T/G_{TU}$ . It can be shown that this ratio is bounded by

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2},\tag{6.48}$$

where U is defined as the unilateral figure of merit,


$$U = \frac{|S_{11}| |S_{12}| |S_{21}| |S_{22}|}{(1 - |S_{11}|^2)(1 - S_{22}|^2)}.$$
(6.49)

Usually an error of a few tenths of a dB or less will justify the unilateral assumption.

The expressions for  $G_S$  and  $G_L$  for the unilateral case are given by (6.20a) and (6.20c):

$$G_{S} = \frac{1 - |\Gamma_{S}|^{2}}{|1 - S_{11}\Gamma_{S}|^{2}},$$
$$G_{L} = \frac{1 - |\Gamma_{L}|^{2}}{|1 - S_{22}\Gamma_{L}|^{2}}.$$

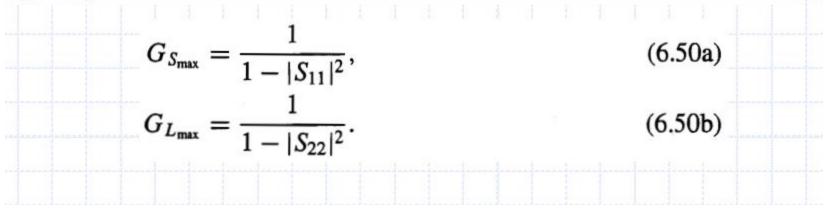These gains are maximized when  $\Gamma_S = S_{11}^*$  and  $\Gamma_L = S_{22}^*$ , resulting in the maximum values given by



Now define the normalized gain factors  $g_S$  and  $g_L$  as

$$g_{S} = \frac{G_{S}}{G_{S_{\text{max}}}} = \frac{1 - |\Gamma_{S}|^{2}}{|1 - S_{11}\Gamma_{S}|^{2}}(1 - |S_{11}|^{2}), \qquad (6.51a)$$
$$g_{L} = \frac{G_{L}}{G_{L_{\text{max}}}} = \frac{1 - |\Gamma_{L}|^{2}}{|1 - S_{22}\Gamma_{L}|^{2}}(1 - |S_{22}|^{2}). \qquad (6.51b)$$

Then we have that  $0 \le g_S \le 1$ , and  $0 \le g_L \le 1$ .

-(

For fixed values of  $g_s$  and  $g_L$ , (6.51) represents circles in the  $\Gamma_s$  or  $\Gamma_L$  plane. To show this, consider (6.51a), which can be expanded to give

$$g_{S}|1 - S_{11}\Gamma_{S}|^{2} = (1 - |\Gamma_{S}|^{2})(1 - |S_{11}|^{2}),$$


$$(g_{S}|S_{11}|^{2} + 1 - |S_{11}|^{2})|\Gamma_{S}|^{2} - g_{S}(S_{11}\Gamma_{S} + S_{11}^{*}\Gamma_{S}^{*}) = 1 - |S_{11}|^{2} - g_{S},$$

$$\Gamma_{S}\Gamma_{S}^{*} - \frac{g_{S}(S_{11}\Gamma_{S} + S_{11}^{*}\Gamma_{S}^{*})}{1 - (1 - g_{S})|S_{11}|^{2}} = \frac{1 - |S_{11}|^{2} - g_{S}}{1 - (1 - g_{S})|S_{11}|^{2}}.$$

$$(6.52)$$

$$\left|\Gamma_{S} - \frac{g_{S}S_{11}^{*}}{1 - (1 - g_{S})|S_{11}|^{2}}\right| = \frac{\sqrt{1 - g_{S}}(1 - |S_{11}|^{2})}{1 - (1 - g_{S})|S_{11}|^{2}},$$

$$(6.53)$$

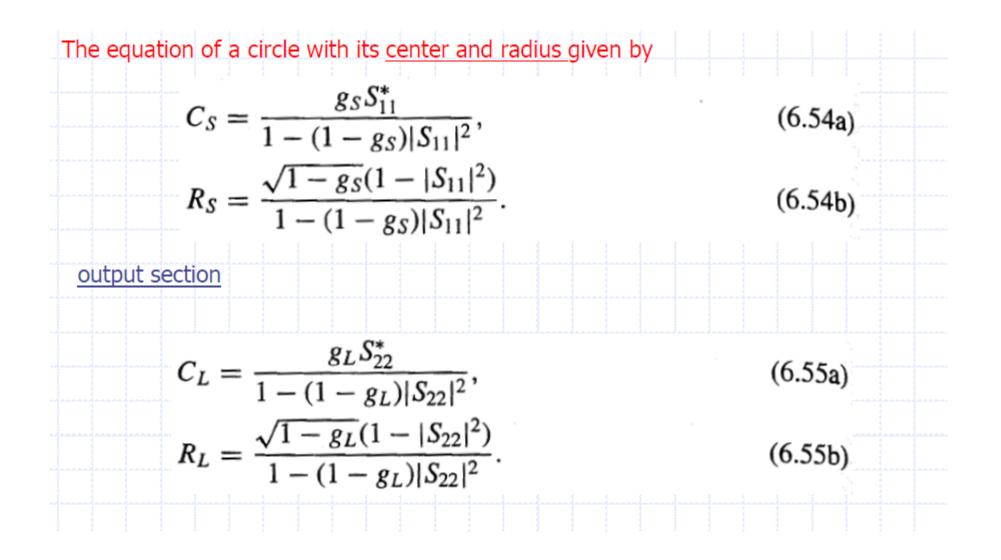

# Summary for the constant gain circles

The centers of each family of circles lie along straight lines given by the angle of  $S_{11}^*$  or  $S_{22}^*$ .

when  $g_s$  (or  $g_L$ ) = 1 (maximum gain), the radius  $R_s$  (or  $R_L$ ) = 0, and the center reduces to  $S_{11}^*$  (or  $S_{22}^*$ )

it can be shown that the 0 dB gain circles

 $(G_S = 1 \text{ or } G_L = 1)$  will always pass through the center of the Smith chart.

The choices for  $\Gamma_S$  and  $\Gamma_L$  are not unique, but it makes sense to choose points close to the center of the Smith chart to minimize the mismatch, and thus maximize the bandwidth. Alternatively, as we will see in the next section, the input network mismatch can be chosen to provide a low-noise design.

#### AMPLIFIER DESIGN FOR SPECIFIED GAIN

Design an amplifier to have a gain of 11 dB at 4.0 GHz. Plot the constant gain circles for  $G_S = 2$  dB and 3 dB, and  $G_L = 0$  dB and 1 dB. Calculate and plot the input return loss and overall amplifier gain from 3 to 5 GHz. Use an FET with the following S parameters ( $Z_0 = 50 \Omega$ ):

f (GHz)	<b>S</b> <sub>11</sub>	$S_{21}$	<i>S</i> <sub>12</sub>	S <sub>22</sub>
3	0.80∠−90°	2.8∠100°	0	0.66∠-50°
4	0.75∠-120°	2.5∠80°	0	0.60∠-70°
5	0.71∠-140°	2.3∠60°	0	0.58∠-85°

Solution

Since  $S_{12} = 0$  and  $|S_{11}| < 1$  and  $|S_{22}| < 1$ , the transistor is unilateral and unconditionally stable. From (6.50) we calculate the maximum matching section gains as

$$G_{S_{\text{max}}} = \frac{1}{1 - |S_{11}|^2} = 2.29 = 3.6 \text{ dB},$$
  
 $G_{L_{\text{max}}} = \frac{1}{1 - |S_{22}|^2} = 1.56 = 1.9 \text{ dB}.$ 

The gain of the mismatched transistor is

$$G_0 = |S_{21}|^2 = 6.25 = 8.0 \text{ dB}$$


so the maximum unilateral transducer gain is


$$G_{TU_{\text{max}}} = 3.6 + 1.9 + 8.0 = 13.5 \text{ dB}.$$

Thus we have 2.5 dB more gain than is required by the specifications. We use (6.51), (6.54), and (6.55) to calculate the following data for the constant gain circles:

 $G_S = 3 \text{ dB}$  $g_S = 0.875$  $C_S = 0.706/120^\circ$  $R_S = 0.166$  $G_S = 2 \text{ dB}$  $g_S = 0.691$  $C_S = 0.627/120^\circ$  $R_S = 0.294$  $G_L = 1 \text{ dB}$  $g_L = 0.806$  $C_L = 0.520/70^\circ$  $R_L = 0.303$  $G_L = 0 \text{ dB}$  $g_L = 0.640$  $C_L = 0.440/70^\circ$  $R_L = 0.440$ 

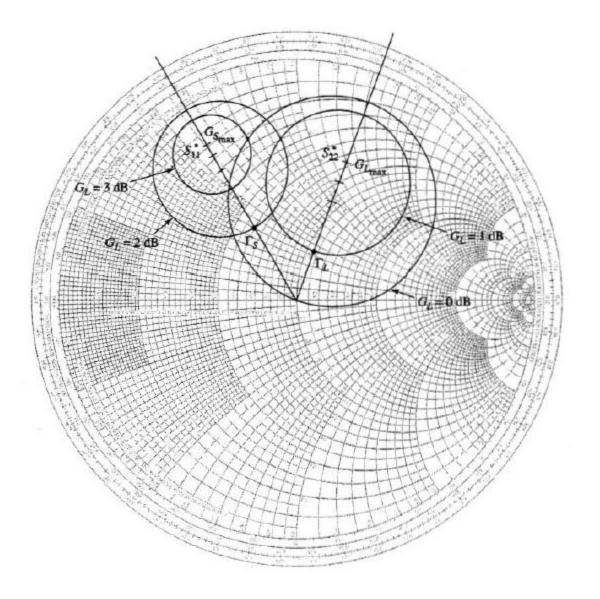The constant gain circles are shown in Figure 6.13a. We can choose  $G_S = 2 \, dB$ and  $G_L = 1 \, dB$ , for an overall amplifier gain of 11 dB. Then we select  $\Gamma_S$  and  $\Gamma_L$ along these circles as shown, to minimize the distance from the center of the chart (this places  $\Gamma_S$  and  $\Gamma_L$  along the radial lines at 120° and 70°, respectively). Thus,



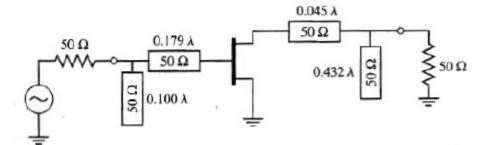

# Example 5

Design an amplifier to have a gain of 11 dB at 4 GHz. Plot constant gain circles for  $G_S = 2$  dB and 3 dB; and  $G_L = 0$  dB and 1 dB. The FET has the following S parameters ( $Z_0 = 50 \Omega$ ):

$$\begin{split} S_{11} &= 0.75 < -120 \\ S_{21} &= 2.50 < 80 \\ S_{12} &= 0.00 < 0 \\ S_{22} &= 0.60 < -85 \end{split}$$

Since  $S_{12} = 0$  and  $|S_{11}| < 1$  and  $|S_{22}| < 1$ , the transistor is unilateral and unconditionally stable. We calculate the max matching section gains as;

$$G_{s_{\text{max}}} = \frac{1}{1 - |S_{11}|^2} = 2.29 = 3.6dB$$
$$G_{L_{\text{max}}} = \frac{1}{1 - |S_{22}|^2} = 1.56 = 1.9dB$$

The gain of the mismatched transistor is;

$$G_{0} = |S_{21}|^{2} = 6.25 = 8.0 dB$$

So the max unilateral transducer gain is


$$G_{T_U \max} = 3.6 + 1.9 + 8.0 = 13.5 dB$$

Thus we have 2.5 dB more available gain than required by specs, since the design only requires 11 dB gain. However, the question also asked us to analyze the effect of having:


Condition 1:  $G_S = 3 \text{ dB}$  and  $G_L = 0 \text{ dB}$ Condition 2:  $G_S = 2 \text{ dB}$  and  $G_L = 1 \text{ dB}$ 


(Note that these conditions must happens at the same time in order to keep the gain at 11 dB.)

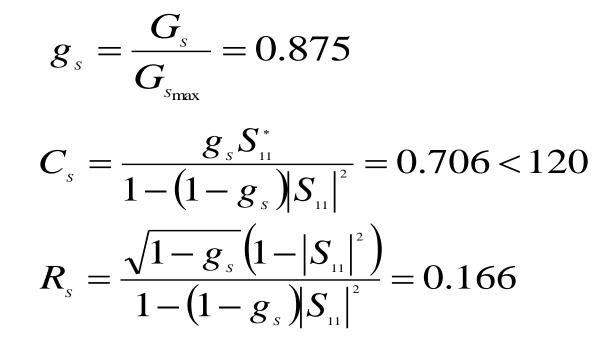For condition 1 (input side), when  $G_S = 3 \text{ dB}$ :



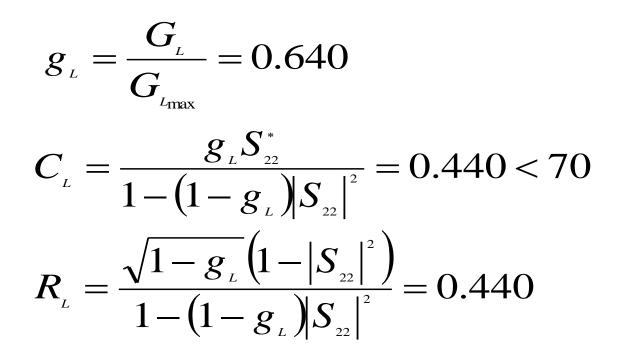
For condition 1 (output side), when  $G_L = 0$  dB:



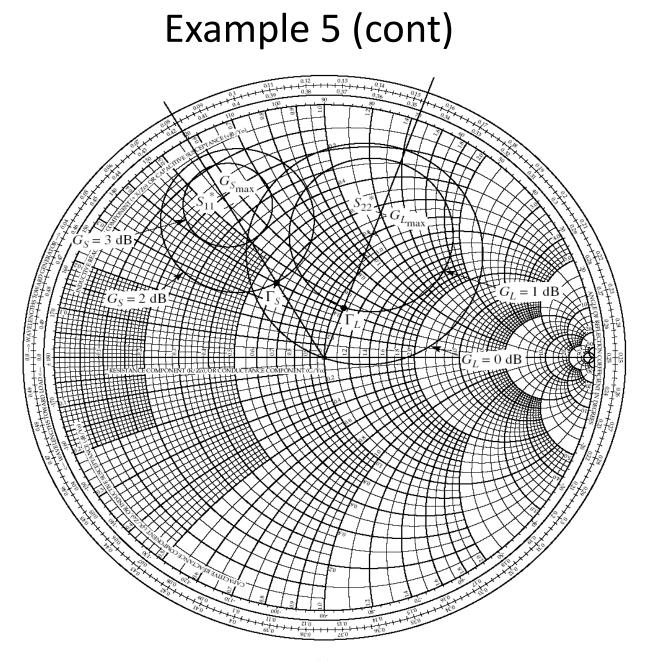
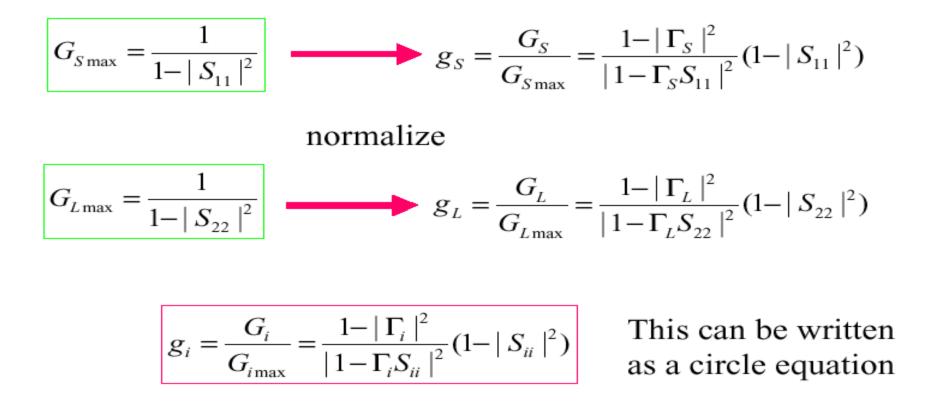
# Constant Gain Circles in the Smith Chart

To obtain desired amplifier gain performance



## **Circle Equation and Graphical Display**


$$(\Gamma_{i}^{R} - d_{g_{i}}^{R})^{2} + (\Gamma_{i}^{I} - d_{g_{i}}^{I})^{2} = r_{g_{i}}^{2}$$

$$d_{g_{i}} = \frac{g_{i}S_{ii}^{*}}{1 - |S_{ii}|^{2}(1 - g_{i})}$$


$$r_{g_{i}} = \frac{\sqrt{1 - g_{i}}(1 - |S_{ii}|^{2})}{1 - |S_{ii}|^{2}(1 - g_{i})}$$

Constant source gain circles

Constant load gain circle

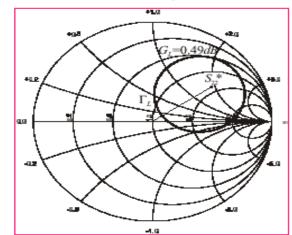



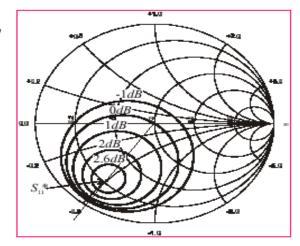


### Gain Circles


- Max gain  $\Gamma_{imax} = 1/(1-|S_{ii}|^2)$  when  $\Gamma_i = S_{ii}^*$ ; gain circle center is at  $d_{gi} = S_{ii}^*$  and radius  $r_{gi} = 0$
- Constant gain circles have centers on a line connecting origin to  $S_{ii}^{*}$
- For special case  $\Gamma_i = 0$ ,  $g_i = 1 |S_{ii}|^2$  and

 $d_{gi} = r_{gi} = |S_{ii}|/(1+|S_{ii}|^2)$  implying  $\Gamma_i = 1$  (0 dB) circle always passes through origin of  $\Gamma_i$  plane

### Trade-off Between Gain and Noise

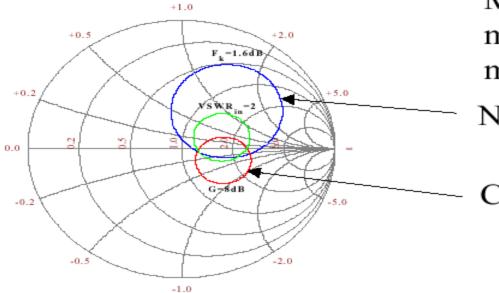

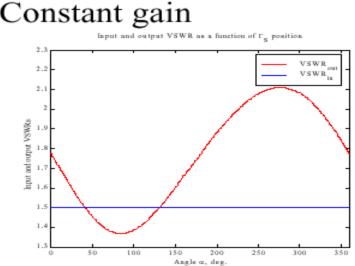Maximum gain and minimum noise figure are mutually exclusive Noise figure



### **Example: Unilateral Constant Gain Circles**

• The s-parameters of a bipolar transistor at 500MHz are the following

S11	S21	S12	S22
0.706 -150deg	3.162 80deg	0.01 45deg	0.866 -60deg

 Compute the coordinates of the lateral consant-gain circles of the source, from G<sub>Smax</sub> to 1dB, in 1 dBsteps, and plot on the Smith Chart.

• 
$$G_{Smax} = \frac{1}{1 - |S_{11}|^2} = \frac{1}{1 - |0.706|^2} = 1.995, \quad 10\log(1.995) = 3dB$$

- Next compute  $g_s$ ,  $C_s$ ,  $r_s$
- $g_s = \frac{G_s}{G_{Smax}} = G_s (1 |S_{11}|^2) = 1.995(1 |0.706|^2) = 1; G_s (\text{in dB}): 3, 2, 1, 0, -1$

• 
$$\Gamma_{s} = S_{11}^{*}$$
  
 $g_{s} = \frac{G_{s}}{G_{s_{\max}}} = \frac{1 - |\Gamma_{s}|^{2}}{|1 - \Gamma_{s}S_{11}|^{2}} (1 - |S_{11}|^{2})$   
 $R_{s} = \frac{\sqrt{1 - g_{s}} (1 - |S_{11}|^{2})}{1 - (1 - g_{s})|S_{11}|^{2}}$ 


## The Corresponding Unilateral Power Gain, with S<sub>12</sub>=0

- If  $S_{12} = 0$ , the maximum gain of a two-port is achieved when  $\Gamma_s = S_{11}^*$  and  $\Gamma_L = S_{22}^*$
- The resultant gain change is,  $G_{Smax} = \frac{1}{1 |S_{11}|^2}$  and  $G_{Lmax} = \frac{1}{1 |S_{22}|^2}$
- The maximum unilateral gain,

$$G_{TUmax} = G_{Smax}G_{omax}G_{Lmax} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

$$G_{TUmaxdB} = G_{SmaxdB} + G_{omaxdB} + G_{LmaxdB}$$

Gs (in dB)	3	2	1	0	-1
Gs(in factor)	2	1.58	1.26	1	0.79
$g_s$	1	0.79	0.63	0.50	0.4
$ C_s $	0.706	0.63	0.55	0.47	0.4
$r_1$	0	0.25	0.37	0.47	0.56

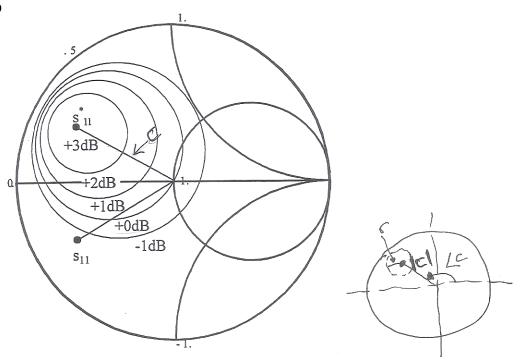


Design and amplifier with 15dB gain, using the transistor specified on the previous pages. Assume unilateral condition and find the appropriate input or output network(s).

1. The basic transducer gain,  $s_{21}=3.16=10$  dB. Therefore +5dB increase is needed.

2. 
$$G_{1 \max} = \frac{1}{1 - |0.706|^2} = 1.995 \Rightarrow 3dB$$
  $G_{2 \max} = \frac{1}{1 - |0.866|^2} = 4 \Rightarrow 6dB$ 

Conjugate matching the input would only increase the gain by 3dB. Achieving a **partial** match at the output can provide +5dB gain increase.

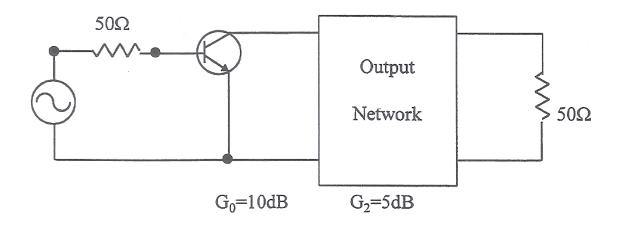- 3. Plot the +5dB unilateral constant gain circle and select the appropriate impedance transforming network (see next page).
- 4. Cascade the output network to the device and compute the total gain.




Computation the +5dB load constant-gain circle:

- 1. Convert +5dB to factor  $G_2 = \log^{-1} \frac{G_{2dB}}{10} = \log^{-1} (0.5) = 3.16$  $g_2 = G_2 (1 - |s_{22}|^2) = 3.16(1 - 0.866^2) = 0.79$
- 2. Compute the center vector


$$C_{2} = \frac{g_{2}s_{22}^{*}}{1 - |s_{22}|^{2}(1 - g_{2})} = \frac{0.79 \cdot (0.866) \cdot (\angle 60^{\circ})^{*}}{1 - 0.866^{2}(1 - 0.79)} = 0.81 \angle 60^{\circ}$$

3. Compute the radius

$$\mathbf{r}_{2} = \frac{\left(1 - |\mathbf{s}_{22}|^{2}\right)\sqrt{1 - \mathbf{g}_{2}}}{1 - |\mathbf{s}_{22}|^{2}\left(1 - \mathbf{g}_{2}\right)} = \frac{\left(1 - 0.866^{2}\right)\sqrt{1 - 0.79}}{1 - 0.866^{2}\left(1 - 0.79\right)} = 0.14$$

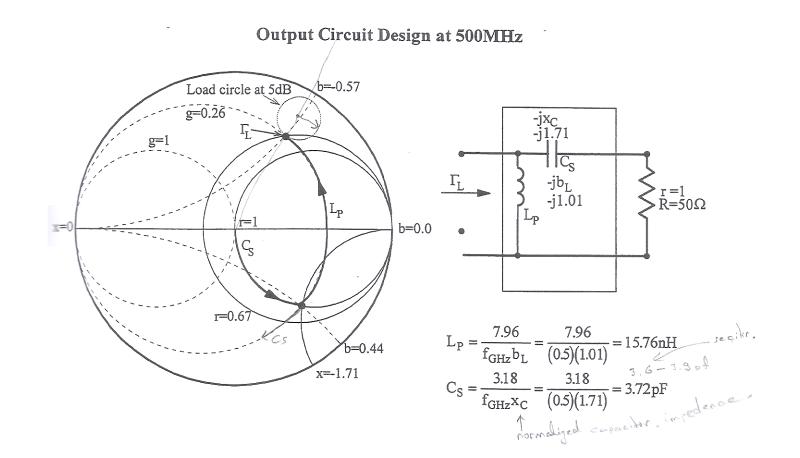

## **Example:** Finish

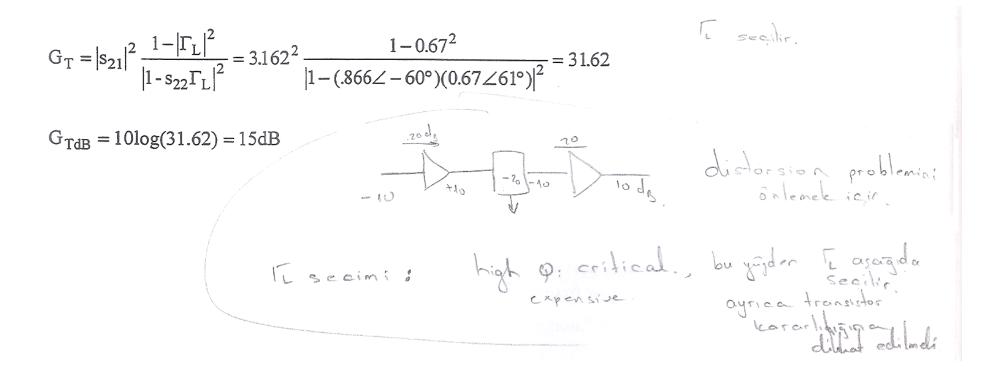


### **Simultaneous Conjugate Match Design**

Simultaneous Conjugate Match Source and Load Terminations

When  $\underline{s_{12}} \neq 0$ , and the unilateral assumption cannot be made, the input and output reflection coefficients are functions of the s-parameters and the termination at the adjacent port. The conditions required to obtain maximum transducer power gain are

$$\Gamma_{\rm MS} = \Gamma_{\rm IN}^*$$
 and  $\Gamma_{\rm ML} = \Gamma_{\rm OUT}^*$ 

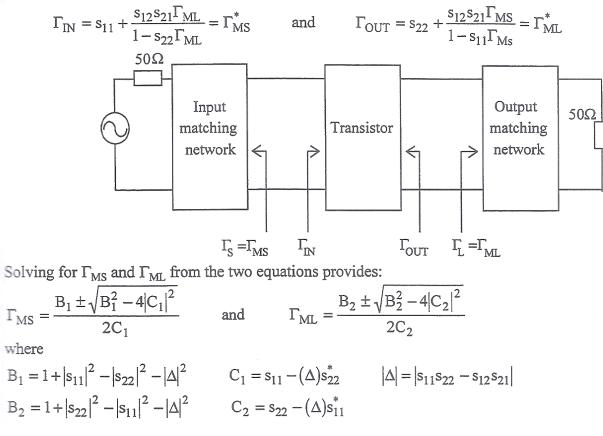
If the above conditions occur simultaneously, the new input output impedances of the devices are:



### **Simultaneous Conjugate Match Maximum Gain**
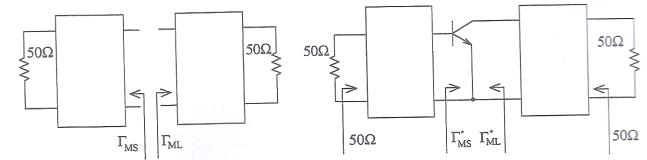
### Simultaneous Conjugate Match Maximum Gain

The matching network may be designed by starting from the  $50\Omega$  terminations or from the transistor.



The maximum transducer power gain, under simultaneous conjugate match conditions, is obtained from the previous transducer gain formula, using  $\Gamma_{S} = \Gamma_{MS}$  and  $\Gamma_{L} = \Gamma_{ML}$ 

$$G_{T,max} = \frac{\left(1 - |\Gamma_{MS}|^{2}\right)|s_{21}|^{2}\left(1 - |\Gamma_{ML}|^{2}\right)}{\left|(1 - s_{11}\Gamma_{MS})(1 - s_{22}\Gamma_{ML}) - s_{21}s_{12}\Gamma_{MS}\Gamma_{ML}}\right|$$

Substituting for  $\Gamma_{MS}$  and  $\Gamma_{ML}$ , and using the stability factor (K), gives the relation


$$G_{T,max} = \frac{|s_{21}|}{|s_{12}|} \left( K - \sqrt{K^2 - 1} \right)$$

The maximum stable gain is as defined the value of  $G_{T,max}$  when K=1, namely

$$G_{MSG} = \frac{|s_{21}|}{|s_{12}|}$$
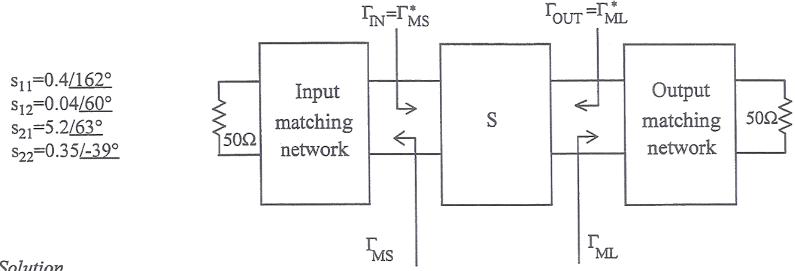
## **Example:Simultaneous Conjugate Match Design**


Find the input and the output networks for the simultaneous conjugate match at 200MHz, for a transistor with the following s-parameters. Use 50 $\Omega$  source and load terminations, and compute the matched gain.



Solution

First see if the transistor is stable at the operating frequency and bias point:

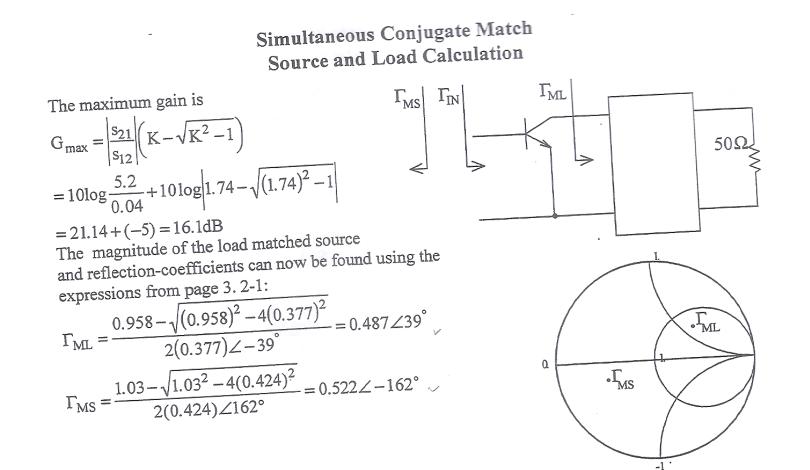
$$K = \frac{1 + (0.068)^2 - (0.4)^2 - (0.35)^2}{2(5.2)(0.04)} = 1.74$$
  
since K is greater than 1, calculate B<sub>1</sub>  
B<sub>1</sub>=1 + (0.4)<sup>2</sup> - (0.35)<sup>2</sup> - (0.068)<sup>2</sup> = 1.03  
The transistor passes both tests, (K > 1, B<sub>1</sub> > 0), therefore at 200MHz it is unconditionally stable



The desired source reflection coefficient,  $\Gamma_{MS} = 0.522 \angle -162^{\circ}$ . Proceeding from the 50 $\Omega$  source, the input matching network is:


Shunt  $C = j1.45 = jb_C$ 

Series  $L = j0.33 = jx_L$ 

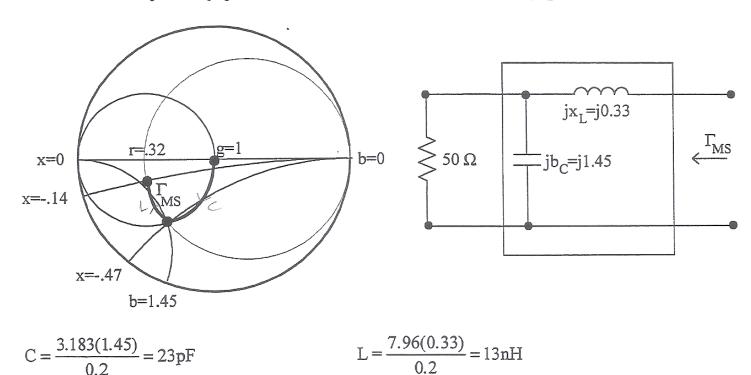

The computed load reflection coefficient,  $\Gamma_{ML} = 0.48 \angle 39^{\circ}$ . The matching output network is designed, proceeding from the 50 $\Omega$  load:

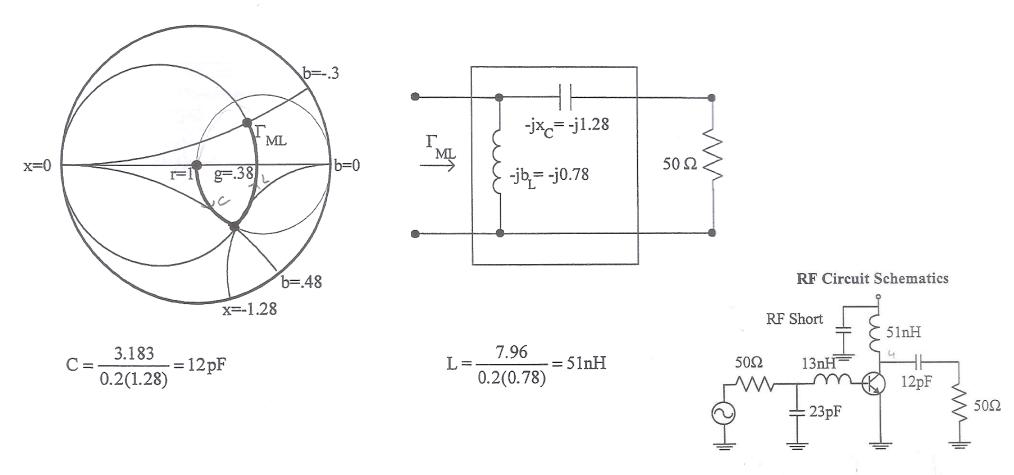Series  $C = -j1.28 = -jx_C$  Shunt  $L = -j0.78 = -jb_L$ 



# **LOW NOISE AMPLIFIER DESIGN**

# Low noise amplifier design

- Besides stability and gain, another important design consideration for an RF or microwave amplifier is its noise figure.
- In receiver applications especially, it is often required to have a preamplifier with as low a noise figure as possible since, the first stage of a receiver front end usually has the dominant effect on the noise performance of the overall system.
- Generally it is not possible to obtain both minimum noise figure and maximum gain for an amplifier, so some sort of compromise must be made.
- This can be done by using constant gain circles and circles of constant noise figure to select a usable trade-off between noise figure and gain.

## Low noise amplifier (LNA) design

the noise figure of a two-port amplifier can be expressed as  $F = F_{\min} + \frac{R_N}{G_S} |Y_S - Y_{opt}|^2,$ (6.56) $Y_S = G_S + jB_S$  = source admittance presented to transistor.  $Y_{opt}$  = optimum source admittance that results in minimum noise figure.  $F_{\min}$  = minimum noise figure of transistor, obtained when  $Y_S = Y_{opt}$ .  $R_N$  = equivalent noise resistance of transistor.  $G_S$  = real part of source admittance. The quantities  $F_{\min}$ ,  $\Gamma_{opt}$ , and  $R_N$ are cnaracteristics of the particular transistor being used, and are called the noise parameters of the device; they may be given by the manufacturer, or measured. Instead of the admittances  $Y_s$  and  $Y_{opt}$ , we can use the reflection coefficients  $\Gamma_s$  and  $\Gamma_{opt}$ , where  $Y_S = \frac{1}{Z_0} \frac{1 - \Gamma_S}{1 + \Gamma_S},$ (6.57a)  $Y_{\rm opt} = \frac{1}{Z_0} \frac{1 - \Gamma_{\rm opt}}{1 + \Gamma_{\rm opt}}.$ (6.57b)

Using (6.57), the quantity  $|Y_S - Y_{opt}|^2$  can be expressed in terms of  $\Gamma_S$  and  $\Gamma_{opt}$ :

$$|Y_{S} - Y_{\text{opt}}|^{2} = \frac{4}{Z_{0}^{2}} \frac{|\Gamma_{S} - \Gamma_{\text{opt}}|^{2}}{|1 + \Gamma_{S}|^{2}|1 + \Gamma_{\text{opt}}|^{2}}.$$
(6.58)

Also,

$$G_{S} = \operatorname{Re}\{Y_{S}\} = \frac{1}{2Z_{0}} \left( \frac{1 - \Gamma_{S}}{1 + \Gamma_{S}} + \frac{1 - \Gamma_{S}^{*}}{1 + \Gamma_{S}^{*}} \right) = \frac{1}{Z_{0}} \frac{1 - |\Gamma_{S}|^{2}}{|1 + \Gamma_{S}|^{2}}.$$
(6.59)

Using these results in (6.56) gives the noise figure as

$$F = F_{\min} + \frac{4R_N}{Z_0} \frac{|\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2)|1 + \Gamma_{opt}|^2}.$$
(6.60)

For a fixed noise figure, F, we can show that this result defines a circle in the  $\Gamma_S$  plane.

First, define the noise figure parameter, N, as

$$N = \frac{|\Gamma_S - \Gamma_{\text{opt}}|^2}{1 - |\Gamma_S|^2} = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{\text{opt}}|^2,$$
(6.61)

which is a constant, for a given noise figure and set of noise parameters. Then rewrite (6.61) as

$$(\Gamma_{S} - \Gamma_{\text{opt}})(\Gamma_{S}^{*} - \Gamma_{\text{opt}}^{*}) = N(1 - |\Gamma_{S}|^{2}),$$
  

$$\Gamma_{S}\Gamma_{S}^{*} - (\Gamma_{S}\Gamma_{\text{opt}}^{*} + \Gamma_{S}^{*}\Gamma_{\text{opt}}) + \Gamma_{\text{opt}}\Gamma_{\text{opt}}^{*} = N - N|\Gamma_{S}|^{2},$$
  

$$\Gamma_{S}\Gamma_{S}^{*} - \frac{(\Gamma_{S}\Gamma_{\text{opt}}^{*} + \Gamma_{S}^{*}\Gamma_{\text{opt}})}{N+1} = \frac{N - |\Gamma_{\text{opt}}|^{2}}{N+1}.$$

Now add  $|\Gamma_{opt}|^2/(N+1)^2$  to both sides to complete the square to obtain

$$\left( \left| \Gamma_{S} - \frac{\Gamma_{\text{opt}}}{N+1} \right| = \frac{\sqrt{N(N+1-|\Gamma_{\text{opt}}|^2)}}{N+1}.$$
(6.62)

This expression defines circles of constant noise figure with centers at

$$C_F = \frac{\Gamma_{\text{opt}}}{N+1},\tag{6.63a}$$

and radii of

$$R_F = \frac{\sqrt{N(N+1-|\Gamma_{\rm opt}|^2)}}{N+1}.$$
 (6.63b)

#### LOW-NOISE AMPLIFIER DESIGN

A GaAs FET is biased for minimum noise figure and has the following S parameters and noise parameters at 4 GHz ( $Z_0 = 50 \Omega$ ):  $S_{11} = 0.60 \angle -60^\circ$ ,  $S_{21} = 1.9 \angle 81^\circ$ ,  $S_{12} = 0.05 \angle 26^\circ$ ,  $S_{22} = 0.5 \angle -60^\circ$ ;  $F_{\min} = 1.6 \text{ dB}$ ,  $\Gamma_{opt} = 0.62 \angle 100^\circ$ ,  $R_N = 20 \Omega$ . For design purposes, assume the device is unilateral, and calculate the maximum error in  $G_T$  resulting from this assumption. Then design an amplifier having a 2.0 dB noise figure with the maximum gain that is possible with this noise figure.

#### Solution

We first compute the unilateral figure of merit from (6.49):

$$U = \frac{|S_{11}||S_{12}||S_{21}||S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} = 0.059.$$

Then from (6.48) the ratio  $G_T/G_{TU}$  is bounded as

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2},$$

or

$$0.891 < \frac{G_T}{G_{TU}} < 1.130.$$

In dB,

$$-0.50 < G_T - G_{TU} < 0.53 \text{ dB},$$

where  $G_T$  and  $G_{TU}$  are now in dB. Thus, we should expect less than about  $\pm 0.5$  dB error in gain due to the approximation of a unilateral device.

Next, we use (6.61) and (6.63) to compute the center and radius of the 2 dB noise figure circle:

$$N = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{opt}|^2 = \frac{1.58 - 1.445}{4(20/50)} |1 + 0.62\angle 100^\circ|^2 = 0.0986,$$

$$C_F = \frac{\Gamma_{opt}}{N+1} = 0.56\angle 100^\circ,$$

$$R_F = \frac{\sqrt{N(N+1-\Gamma_{opt}|^2)}}{N+1} = 0.24.$$

This noise figure circle is plotted in Figure 6.14a. Minimum noise figure  $(F_{\min} = 1.6 \text{ dB})$  occurs for  $\Gamma_S = \Gamma_{opt} = 0.62 \angle 100^\circ$ . Next, we calculate data for

several input section constant gain circles. From (6.54) we compute the following data:

$G_{s}$ (dB)	<b>8</b> 5	$C_{S}$	R <sub>s</sub>
1.0	0.805	0.52∠60°	0.300
1.5	0.904	0.56∠60°	0.205
1.7	0.946	0.58∠60°	0.150

These circles are also plotted in Figure 6.14a. We see that the  $G_s = 1.7$  dB gain

circle just intersects the F = 2 dB noise figure circle, and that any higher gain will result in a worse noise figure. From the Smith chart the optimum solution is then  $\Gamma_S = 0.53 \angle 75^\circ$ , yielding  $G_S = 1.7$  dB and F = 2.0 dB.

For the output section we chose  $\Gamma_L = S_{22}^* = 0.5 \angle 60^\circ$  for a maximum  $G_L$  of

$$G_L = \frac{1}{1 - |S_{22}|^2} = 1.33 = 1.25 \text{ dB}.$$


The transistor gain is

$$G_0 = |S_{21}|^2 = 3.61 = 5.58 \text{ dB}.$$

so the overall transducer gain will be

$$G_{TU} = G_S + G_0 + G_L = 8.53 \text{ dB}.$$

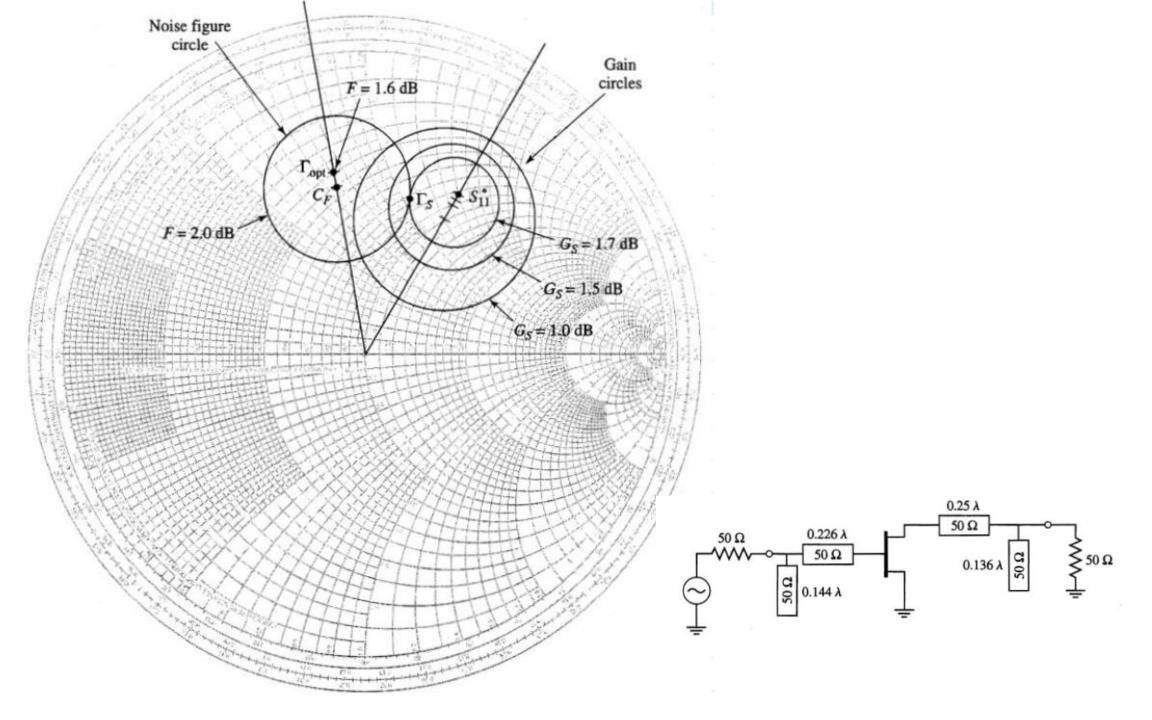The complete AC circuit for the amplifier, using open-circuited shunt stubs in the matching sections, is shown in Figure 6.14b. A computer analysis of the circuit (with  $S_{12} \neq 0$ ) gave a gain of 8.36 dB.



## Example 6

An GaAs FET amplifier is biased for minimum noise figure and has the following S-parameters ( $Z_0 = 50 \Omega$ ):

$$\begin{split} S_{11} &= 0.75 < -120 \\ S_{21} &= 2.50 < 80 \\ S_{12} &= 0.00 < 0 \\ S_{22} &= 0.60 < -85 \\ \Gamma_{opt} &= 0.62 < 100 \\ F_{min} &= 1.6 \text{ dB} \\ R_N &= 20 \text{ }\Omega \end{split}$$

For design purposes, assume the unilateral. Then design an amplifier having 2.0 dB noise figure with the max gain that is compatible with this noise figure.

Next use the formulas to compute the center and radius of the 2 dB noise figure circle:

$$N = \frac{F - F_{min}}{4R_{N}/Z_{0}} \left| 1 - \Gamma_{opt} \right|^{2} = 0.0986$$

$$C_{F} = \frac{\Gamma_{opt}}{N+1} = 0.56 < 100$$
$$R_{F} = \frac{\sqrt{N(N+1-|\Gamma_{opt}|^{2})}}{N+1} = 0.24$$

The gain of the mismatched transistor is


The noise figure circle is plotted in the figure. Min noise figure ( $F_{min} = 1.6 \text{ dB}$ ) occurs for  $\Gamma_S = \Gamma_{opt} = 0.62 < 100^{\circ}$ 

$G_{s}(dB)$	gs	C <sub>S</sub>	R <sub>S</sub>
1.0	0.805	0.52<60°	0.300
1.5	0.904	0.56<60°	0.205
1.7	0.946	0.58<60°	0.150


It can be seen that  $G_S = 1.7$  dB gain circle just intersects the F = 2.0 dB noise figure circle, and any higher gain will result in a worse noise figure.

For the output section we choose  $\Gamma_L = S_{22}^* = 0.5 < 60^\circ$  for a max  $G_L$  of:

$$G_{L} = \frac{1}{1 - |S_{22}|^{2}} = 1.33 = 1.25 dB$$
$$G_{0} = |S_{21}|^{2} = 3.61 = 5.58 dB$$
$$G_{U} = G_{S} + G_{0} + G_{L} = 8.53 dB$$

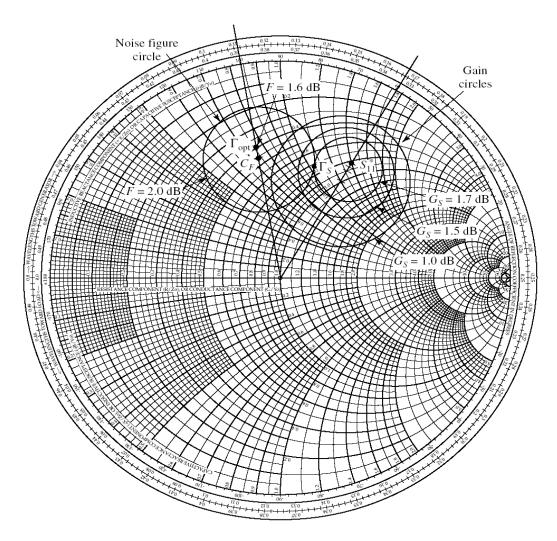

# Examples

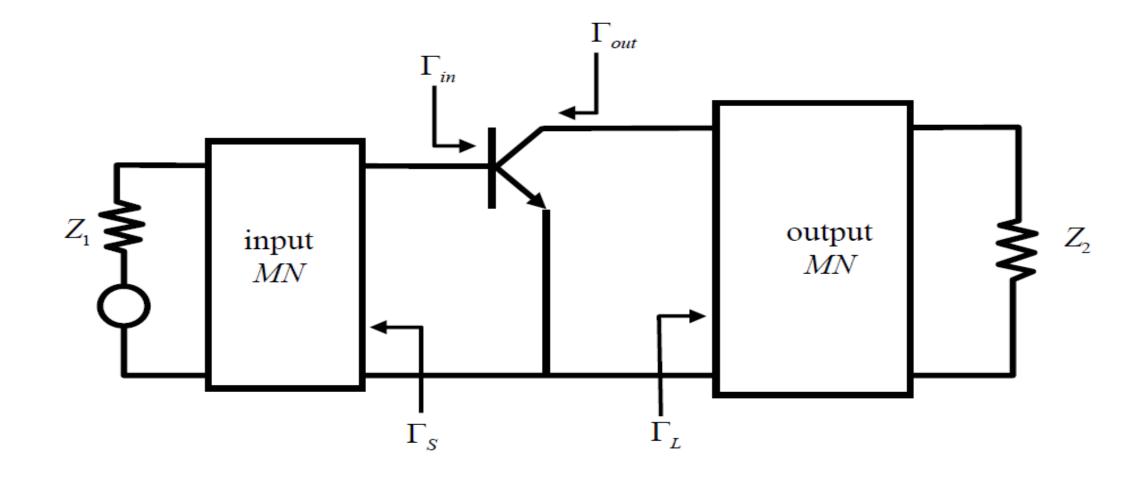

A silicon transitor has following S-matrix at 1 GHz with a  $50\Omega$  reference impedance,

 $\begin{bmatrix} 0.38 \angle -158^0 & 0.01 \angle 34^0 \\ 3.50 \angle 80^0 & 0.40 \angle -43^0 \end{bmatrix}$ 

The source and load impedances are  $25\Omega$  and  $40\Omega$  respectively. Compute the unilateral power gain, unilateral available power gain and unilateral transducer power gain.

### Solution:

From the S-matrix, it is obvious that, the transistor has  $S_{12} = 0.01 \angle 34^0$  which is comparatively small and closes to zero. Hence, it can be assumed that the transistor is unilateral.

The value of source reflection coefficient  $\Gamma_s$  and load reflection coefficient  $\Gamma_l$  can be calculated as

$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3} = \frac{1}{3} \angle 180^0$$
$$\Gamma_l = \frac{Z_l - Z_0}{Z_l - Z_0} = \frac{40 - 50}{40 + 50} = -\frac{1}{9} = \frac{1}{9} \angle 180^0$$

From the generic formula we can calculate the power gain of the transistor,

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_l|^2)}{(1 - |\Gamma_{in}|^2)|1 - S_{22}\Gamma_l|^2}$$

Now, as the transistor is approximated as unilateral, therefore,  $\Gamma_{out} \approx S_{22}$  and  $\Gamma_{in} \approx S_{11}$ . So,

$$G = G_U = \frac{|S_{21}|^2 (1 - |\Gamma_l|^2)}{(1 - |S_{11}|^2)|1 - S_{22}\Gamma_l|^2}$$
$$= \frac{(3.50)^2 \times 0.99}{0.86 \times [1 - 0.05 \angle 137^0]^2}$$
$$= \frac{3.5^2 \times 0.99}{0.86 \times 1.08}$$
$$= 13.05$$
$$= 11.16 dB$$

Similarly by applying the generic formula of available power gain as given below, the required


parameter can be calculated.

$$\begin{split} G_A &= G_{AU} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11} \Gamma_s|^2 (1 - |S_{22}|^2)} \\ &= \frac{3.5^2 \times 0.89}{0.84 \times |1 - 0.13 \angle 27^0|^2} \\ &= \frac{3.5^2 \times 0.89}{0.84 \times 0.79} = 16.49 = 12.15 dB \end{split}$$

In similar fashion,

$$G_T = G_{TU} = \frac{|S_{21}|^2 [1 - |\Gamma_s|^2] [1 - \Gamma_l]^2}{|1 - S_{11} \Gamma_s|^2 |1 - S_{22} \Gamma_l|^2}$$
  
=  $\frac{3.5^2 \times 0.99 \times 0.89}{|1 - 0.13 \angle 27^0|^2 |1 - 0.05 \angle 137^0|^2}$   
=  $\frac{3.5^2 \times 0.99 \times 0.89}{0.79 \times 1.08} = 12.65 = 11.02 dB$ 

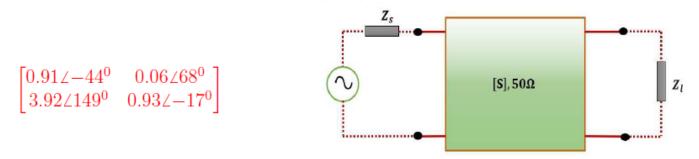A transistor has following S matrix at 1 GHz (50 $\Omega$ ) and connected to the network given below.



Determine the value of  $\Gamma_s$  and  $\Gamma_l$  to maximize the transducer power gain. Solution:

We need to determine the values  $\Gamma_s$  and  $\Gamma_l$  such that the transducer gain is maximum. Therefore, at first we need to check the stability of the transistor.

By applying the Rollet's stability criteria,

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$$

where  $\triangle = S_{11}S_{22} - S_{12}S_{21}$  and  $|\triangle| = |0.91\angle -44^{0}0.93\angle -17^{0} - 3.92\angle 149^{0}0.06\angle 68^{0}| = |0.6 - j0.6| = 0.84 < 1$ . Hence,

$$K = \frac{1 - 0.91^2 - 0.93^2 + 0.84^2}{2 \times 3.92 \times 0.06}$$
  
= 0.026  
< 1

As the transistor fails the Rollet's stability test, the transistor network will be conditionally stable for some values of  $Z_s$  and  $Z_l$ . Therefore, we need to determine the range of values  $\Gamma_l$  and  $\Gamma_s$  for which the transistor network will be stable. We need to determine the centers and radii of input and output stability circles.

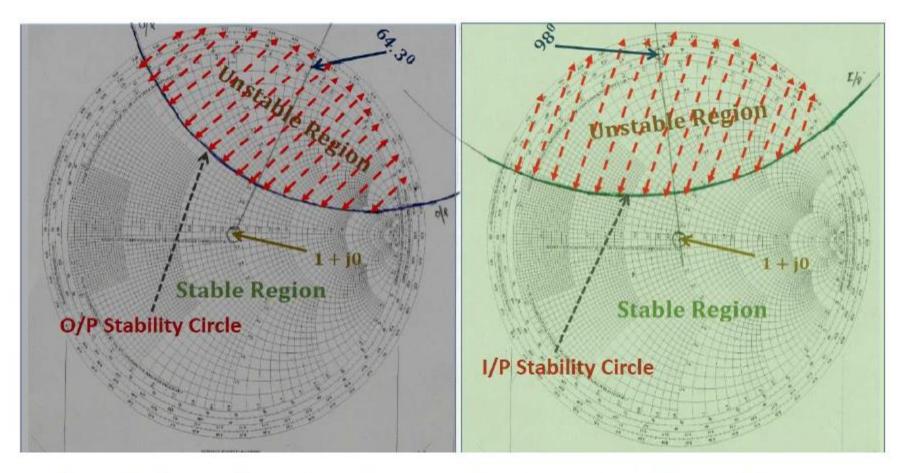


Figure 1: The stable and unstable regions for a transistor with specific S-matrix

$$C_{l} = \frac{(S_{22} - \triangle S_{11}^{*})^{*}}{|S_{22}^{2}| - |\triangle|^{2}}$$
$$= \frac{0.93\angle -17^{0} - (0.84\angle -45^{0} \times 0.91\angle 44^{0})}{0.93^{2} - 0.84^{2}} = 0.78 + j1.62 = 1.8\angle 64.3^{0}$$

$$R_l = \frac{|S_{12}S_{21}|}{|S_{22}^2| - |\Delta|^2} = \frac{0.235}{0.93^2 - 0.84^2} = 1.48$$

$$C_s = \frac{(S_{11} - \triangle S_{22}^*)^*}{|S_{11}^2| - |\triangle|^2}$$
  
=  $\frac{0.91\angle -44^0 - (0.84\angle -45^0 \times 0.93\angle 17^0)}{0.91^2 - 0.84^2}$   
=  $-0.29 + j2.17 = 2.19\angle 97.6^0$   
 $R_s = \frac{|S_{12}S_{21}|}{|S_{11}^2| - |\triangle|^2}$   
=  $\frac{0.235}{0.91^2 - 0.84^2} = 1.92$ 

The input stability circle divides the smith chart into two parts. The region of stability can be determined by considering the valued of  $|S_{11}|$ . If  $|S_{11}| < 1$ , then the region containing the center of the smith chart will be stable region for both input stability circle case (i.e. load reflection

coefficient) and output stability circle case (i.e. source reflection coefficient).

Same recipe can be applied for identifying the stable region for output side but the decision has to be taken based on the value  $|S_{22}|$ . In the present case the  $|S_{11}| < 1$  and  $|S_{22}| < 1$ , thus, the portion of smith chart containing the center will be stable region. The stable and unstable regions are determined using Smith chart and shown in Figure-1.

Now, 
$$\Gamma_s = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$
 and  $\Gamma_l = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$ . Where,  
 $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 = 0.257$   
 $B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 = 0.331$   
 $C_1 = S_{11} - \Delta S_{22}^*$   
 $= 0.91\angle -44^0 - (0.84\angle -45^0 \times 0.93\angle 17^0)$   
 $= -0.03 - 0.27j = 0.27\angle -96.3^0$ 

In order to have a solution of  $\Gamma_l$  and  $\Gamma_s$  for conjugate matching, the quantities,  $B_1^2 - 4|C_1|^2$  and  $B_1^2 - 4|C_1|^2$  must have positive values. In this case, none of the quantities gives a positive value. Therefore, the maximum gain can not be obtained and the transistor network can not be matched to achieve the maximum gain.

An amplifier uses a GaAs HBT device having the following scattering parameters ( $Z_0 = 50\Omega$ ). The input of the transistor is connected to a source with  $V_s = 2V$ (peak) and  $Z_s = 25\Omega$  and the output is connected to  $Z_l = 100\Omega$  load. Compute the available power from the source and power delivered to the load.

$0.61 \angle -170^{\circ}$	$0.06 \angle 70^{\circ}$
$2.3 \angle 80^{0}$	$\begin{array}{c} 0.06\angle70^{0} \\ 0.72\angle-25^{0} \end{array}$

### Solution:

The reflection coefficients  $\Gamma_s$  and  $\Gamma_l$  can be determined as

$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3} = \frac{1}{3} \angle 180^0$$
$$\Gamma_l = \frac{Z_l - Z_0}{Z_l + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

From the signal flow graph, the value of input and output reflection coefficients can be determined as

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_l}{1 - S_{22}\Gamma_l}$$
  
=  $0.61\angle -170^0 + \frac{2.3\angle 80^0 \times 0.6\angle 70^0 \times \frac{1}{3}}{1 - 0.72\angle -25 \times \frac{1}{3}} = -0.65 - j0.07 = 0.65\angle -173.77^0$ 

$$\begin{split} \Gamma_{out} &= S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \\ &= 0.72\angle -25^0 + \frac{2.3\angle 80^0 \times 0.6\angle 70^0 \times \frac{1}{3}\angle 180^0}{1 - 0.61\angle -170^0 \times \frac{1}{3}\angle 180^0} = 0.703 - j0.33 = 0.776\angle -25^0 \end{split}$$

Now, the average power supplied by the source to the transistor network is

$$P_{s} = \frac{1}{2Z_{0}} |V^{+}|^{2}$$

$$= \frac{|V_{s}|^{2}}{8Z_{0}} \frac{|1 - \Gamma_{s}|^{2}}{|-\Gamma_{s}\Gamma_{in}|^{2}}$$


$$= \frac{2}{8 \times 50} \times \frac{|1 - \frac{1}{3}\angle 180^{0}|^{2}}{|1 - (\frac{1}{3}\angle 180^{0} \times 0.65\angle -173^{0})|^{2}}$$

$$= 0.014W$$

In similar fashion, the power delivered to the load can be determined as

$$\begin{split} P_l &= \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_l|^2) |1 - \Gamma_s|^2}{|1 - S_{22}\Gamma_l|^2 |1 - \Gamma_s\Gamma_{in}|^2} \\ &= \frac{2}{8 \times 50} \times \frac{2.3^2 \times (1 - \frac{1}{9}) \times |1 - \frac{1}{3} \angle 180^0|^2}{|1 - 0.72 \angle -25^0|^2 \times |1 - (13 \angle 180^0 \times 0.65 \angle -173.77^0)|^2} \\ &= 0.108W \end{split}$$

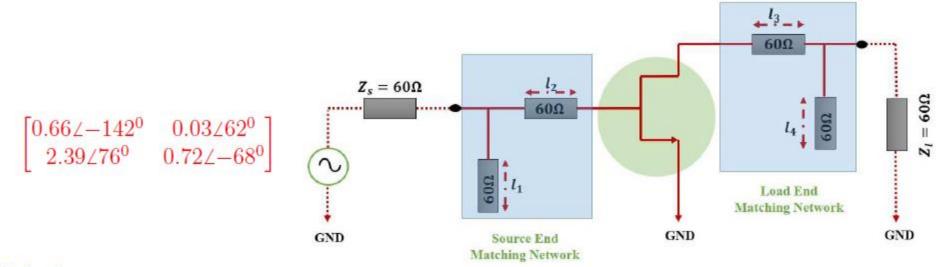Determine the length of short-circuited shunt stubs  $(l_1 \text{ and } l_4)$  & the length of the transmission line  $(l_2 \text{ and } l_3)$  at 3 GHz for the network shown below. The s-matrix of the network is.



### Solution:

The transmission lines used in the matching networks are assumed to be lossless. In order to design the matching network, we need to check the stability conditions of the transistor from the supplied S-matrix values.

Applying Rollet's stability criteria we get

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$$


where  $\triangle = S_{11}S_{22} - S_{12}S_{21}$  and  $|\triangle| = |0.66 \angle -142^0 0.72 \angle -68^0 - 2.39 \angle 54^0 0.03 \angle 62^0| = |-0.38 + j.173| = 0.42 < 1$ . Hence,

$$K = \frac{1 - 0.66^2 - 0.72^2 + 0.42^2}{2 \times 2.39 \times 0.03} = 1.55 > 1$$

Therefor, the transistor network passes the Rollet's stability criteria. So, the network is absolutely stable for any values of  $\Gamma_s$  and  $\Gamma_l$ .

Hence, 
$$\Gamma_s = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$
 and  $\Gamma_l = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$ . Where,  
 $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 = 0.74$   
 $B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 = 0.91$   
 $C_1 = S_{11} - \Delta S_{22}^* = -0.3 - 0.198j$   
 $C_2 = S_{22} - \Delta S_{11}^* = 1.98 \times 10^{-4} - j0.73$ 

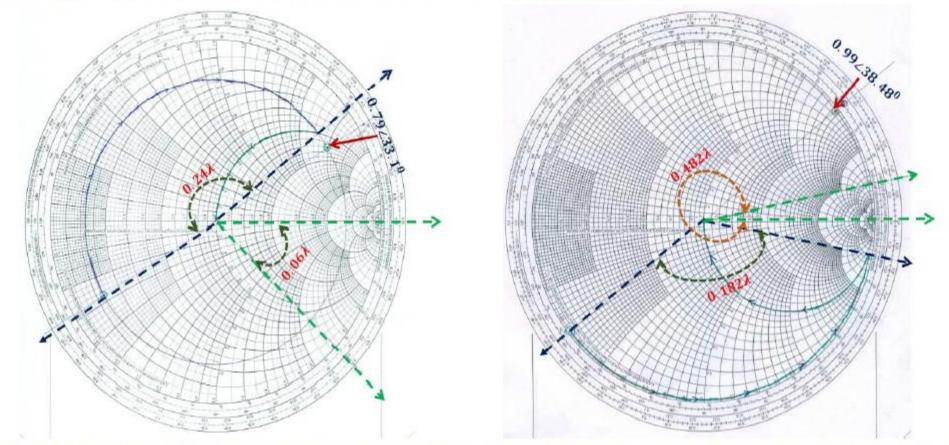So,  $\Gamma_s = 0.78 + 0.62j = 0.79 \angle 33.1^0$  and  $\Gamma_l = 0.78 + 0.62j = 0.99 \angle 38.48^0$ . The length of the short circuited shunt stubs and the length of the transmission line can be easily determined by using Smith chart. Smith chart based solutions for the same are shown below.



Smith Chart based solution for input matching Smith Chart based solution for output matching network network

It is mentioned in the problem that all the values are taken at a frequency of 3 GHz. Hence, the value of wavelength  $\lambda = \frac{3 \times 10^{10}}{3 \times 10^9} = 10$  cm.

So, the length of the short circuited stubs  $l_1 = 0.06\lambda = 0.6$ cm,  $l_4 = 0.182\lambda = 1.82$ cm, and the length of the lossless transion lines are  $l_2 = 0.24\lambda = 2.4$  cm and  $l_3 = 0.482\lambda = 4.82$ cm. The entire transistor network after conjugate matching is shown in Figure-2

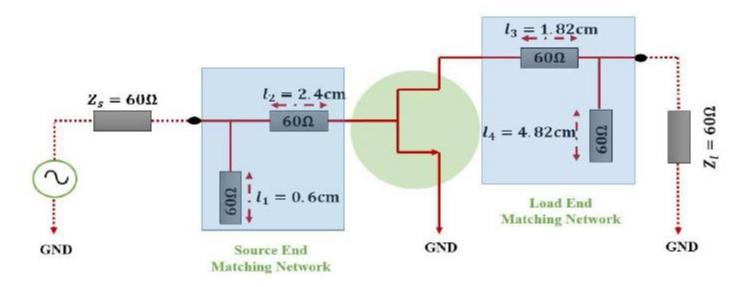


Figure 2: A transistor network with conjugate matching sections

# Kaynaklar

- <a href="https://www.ece.ucsb.edu/~long/ece145a/ampdesign.pdf">https://www.ece.ucsb.edu/~long/ece145a/ampdesign.pdf</a>
- Amplifiers, Prof. Tzong-Lin Wu. EMC Laboratory. Department of Electrical Engineering. National Taiwan University



- These slides were gathered from the presentations published on the internet. I would like to thank who prepared slides and documents.
- Also, these slides are made publicly available on the web for anyone to use
- If you choose to use them, I ask that you alert me of any mistakes which were made and allow me the option of incorporating such changes (with an acknowledgment) in my set of slides.

Sincerely, Dr. Cahit Karakuş cahitkarakus@gmail.com